

Book

Q.10 for $s=0 \rightarrow F = A+B$.
 " $s=1 \rightarrow F = A+1$

So,


S	X	Y	Z _{in}	F
0	A	B	0	A+B
1	A	0	1	A+1

So, $X = AS + AS' = A(S+S') = A$.

$$Y = S'B$$

$$Z = S$$

Design

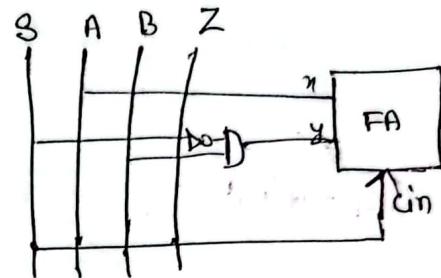

Q.11 Said that $F = A - B$ produces correct difference if $A \geq B$
 and because $A - B \geq 2^n$ then $Cout = 1$

$$\Rightarrow A + \bar{B} + 1 \geq 2^n$$

$$\Rightarrow A - B + 2^n - 1 \geq 2^n$$

$$\Rightarrow A \geq B$$

So when $A < B$ which means the difference will give borrow.

1. the result will be $A - B - 1 \geq 2^n$

$$\Rightarrow A + \bar{B} \geq 2^n$$

$$\Rightarrow A - B + 2^n - 1 \geq 2^n$$

$\Rightarrow A \geq B + 1$ Which means there will be a borrow 1.

The relationship between F and a borrow in the most significant position is $A \geq B + 1$.

Q.12


S	S ₀	Cin	A _n	Y	Z	F
0	0	0	A	B	0	A+B
0	1	0	A	0	0	A
1	0	0	\bar{B}	0	0	\bar{B}
1	1	0	A	\bar{B}	0	$A + \bar{B}$
0	0	1	A	\bar{B}	1	$A + B + 1$
0	1	1	A	0	1	$A + 1$
1	0	1	\bar{B}	0	1	$\bar{B} + 1$
1	1	1	A	\bar{B}	1	$A + \bar{B} + 1$

$$Z = C_{in};$$

$$X_i = S_1' A + S_1 S_0 A + S_1 S_0' B'$$

$$Y_i = S_1' S_0' B + S_1 S_0 \bar{B}$$

$$= S_1 S_0 \oplus \bar{B} B$$

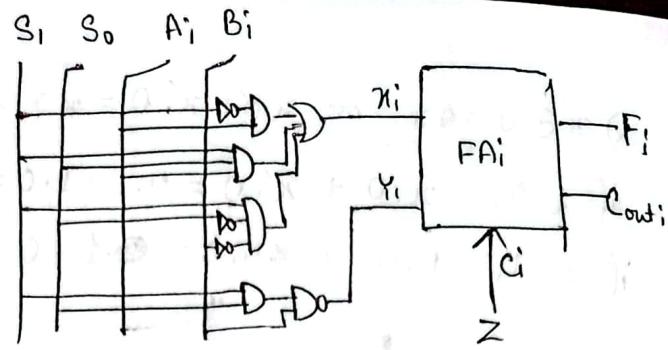


Q.13

S ₁	S ₀	C _{in}	X	Y	Z	F
0	0	0	A	0	0	A
0	1	0	A	\bar{B}	0	$A - B - 1$
1	0	0	B	\bar{A}	0	$B - A - 1$
1	1	0	A	B	0	$A + B$
0	0	1	A	0	1	$A + 1$
0	1	1	A	\bar{B}	1	$A - B$
1	0	1	B	\bar{A}	1	$B - A$
1	1	1	A	B	1	$A + B + 1$

$$Z = C_i$$

$$X_i = S_1' A + S_1 S_0 A + S_1 S_0' B$$
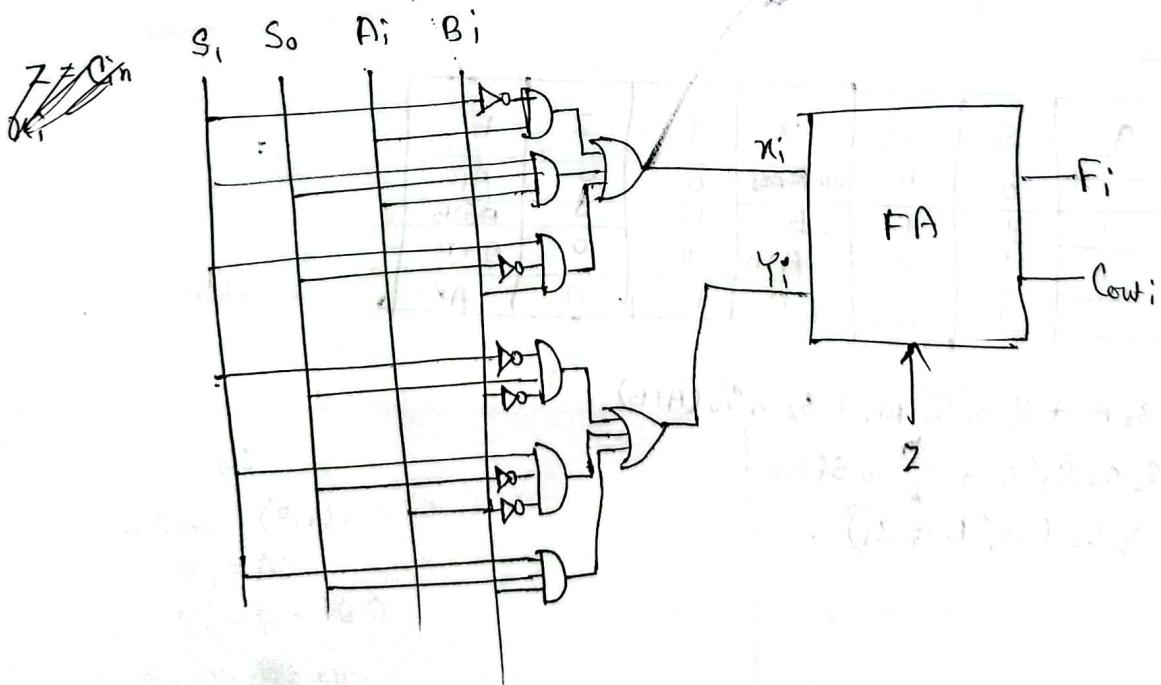
$$Y_i = S_1' S_0' B + S_1 S_0 \bar{B} + S_1 S_0 B$$



9.14

$$a) x \oplus 0 = x, \text{ or, } x \cdot 0' + x' \cdot 0 = x$$

$$\text{if } x=0; \quad x \cdot 0' + x' \cdot 0 = 0 \cdot 1 + 1 \cdot 0 = 0.$$

$$\text{if } x=1; \quad 1 \cdot 0' + 0 \cdot 0 = 1 \cdot 1 + 0 = 1.$$

$$b) x \oplus 1 = x' \text{ which means, } x \cdot 1' + x' \cdot 1 = x'$$

$$\text{if } x=0; \quad 0 \cdot 1' + 0' \cdot 1 = 0 \cdot 0 + 1 \cdot 1 = 1.$$

$$\text{if } x=1; \quad 1 \cdot 1' + 1' \cdot 1 = 0 + 0 = 0.$$

$$c) x \oplus y' = x(y')' + x'y'$$

$$= xy + x'y'$$

$$= x \odot y. \quad (\text{Proved})$$

9.16

S_2	S_1	S_0	x	y	z	F
1	0	0	AB	0	0	AB
1	0	1	$A \oplus B$	0	0	$A \oplus B$
1	1	0	$A+B$	0	0	$A+B$
1	1	1	A'	0	0	A'


9.16

S_2	S_1	S_0	x	y	z	F
1	0	0	AB	0	0	AB
1	0	1	A	B	0	$B \oplus B$
1	1	0	$A+B$	0	0	$A+B$
1	1	1	A	1	0	A'

$$x = S_2 A + S_2 S_1 S_0' AB + S_2 S_1 S_0' (A+B)$$

$$y = S_2 S_0 S_1' B + S_2 S_0 S_1$$

$$= S_2 S_0 (S_1' B + S_1)$$

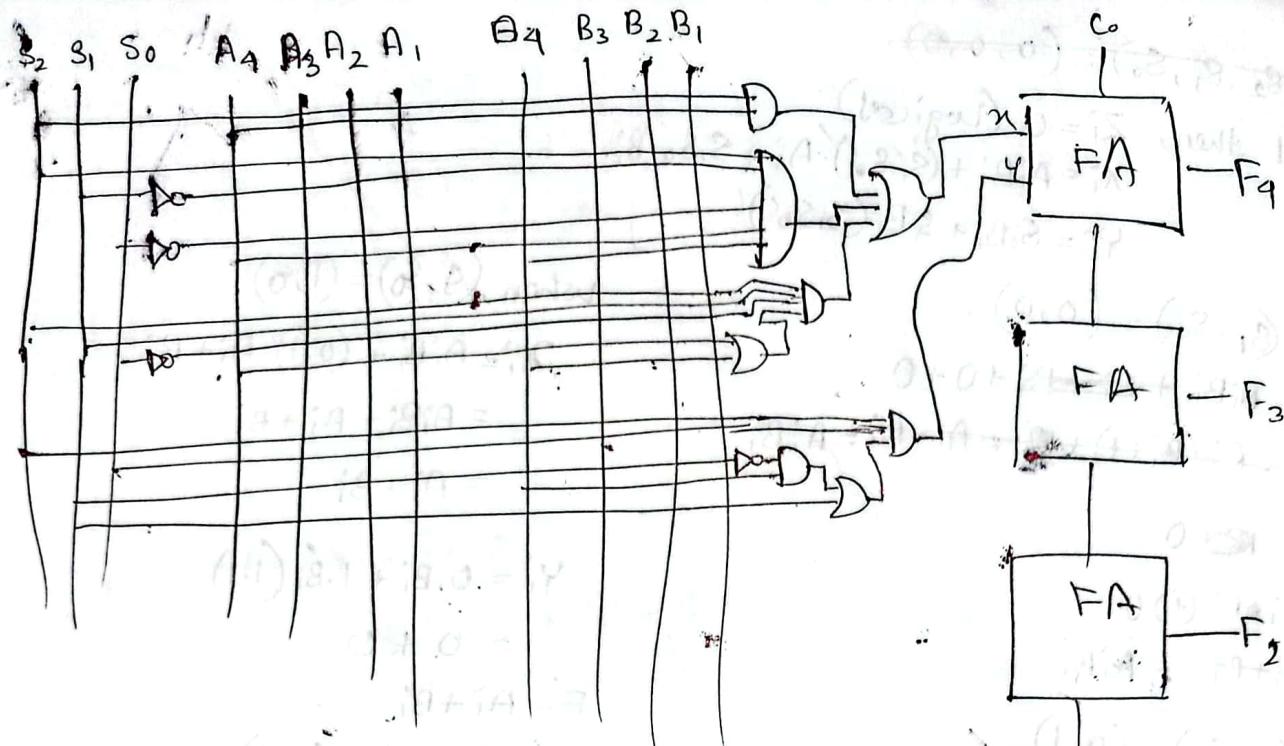

যাকি মূল কণা লাগিবে

9.17

$$\text{Given, } z_i = S_2' C_i$$

$$x_i = A_i B_i + (S_2 S_1' S_0')' A_i + S_2 S_1 S_0' B_i$$

$$y_i = S_0 B_i + S_1 B_i (S_2 S_1 S_0')'$$

if $S_2 = 0$, then $z_i = C_i$ (arithmetic)

$$\text{again } (S_1, S_0) = (0, 0) \cdot x_i = A_i B_i + (0, S_1' S_0')' A_i + 0, S_1 S_0' B_i$$

$$= A_i B_i + A_i + 0 = A_i$$

$$y_i = S_0 B_i + S_1 B_i (0, S_1 S_0')'$$

$$= S_0 B_i + S_1 B_i$$

$$\text{when, } (S_1, S_0) = (0, 0)$$

$$x_i = A_i$$

$$y_i = 0, B_i + 0, B_i' = 0 \cdot i$$

$$F = A_i$$

$$\text{when, } (S_1, S_0) = (0, 1)$$

$$x_i = A_i$$

$$y_i = B_i + \cancel{B_i} = 0$$

$$F = A_i + \cancel{B_i} + B_i$$

$$\text{when } (S_1, S_0) = (1, 0)$$

$$x_i = A_i$$

$$y_i = 0 + B_i'$$

$$F = A_i + \overline{B_i}$$

$$\text{when } (S_1, S_0) = (1, 1)$$

$$x_i = A_i$$

$$y_i = B_i + B_i' = 1$$

$$F = A_i + 1 \cdot 1$$

If $(S_2, S_1, S_0) = (0, 0, 0)$

If $S_2 = 1$ then, $Z_i = 0$. (logical)

$$X_i = A_i B_i + (S_1 S_0)' A_i + S_1 S_0 B_i$$

$$Y_i = S_0 B_i + S_1 B_i (S_1 S_0)'$$

when, $(S_1, S_0) = (0, 0)$

$$X_i = A_i B_i + \cancel{A_i} + \cancel{B_i} + 0 + 0$$

$$\Rightarrow A_i (B_i + 1) + 0 = A_i + B_i = A_i B_i$$

$$Y_i = \cancel{B_i} 0$$

$$F = A_i B_i \oplus 0$$

$$= \cancel{A_i + B_i} = A_i B_i$$

when, $(S_1, S_0) = (0, 1)$

$$X_i = A_i B_i + (1, 0)' A_i + 0, 0, B_i$$

$$\Rightarrow A_i B_i + A_i = A_i$$

$$Y_i = B_i + 0, B_i' (0, 0)'$$

$$= B_i$$

$$F = A_i \oplus B_i$$

when, $(S_1, S_0) = (1, 0)$

$$X_i = A_i B_i + (0, 1)' A_i + B_i$$

$$= A_i B_i + A_i + B_i$$

$$= A_i + B_i$$

$$Y_i = 0, B_i + 1, B_i' (1, 1)'$$

$$= 0 + 0$$

$$F = A_i + B_i$$

when, $(S_1, S_0) = (1, 1)$

$$X_i = A_i B_i + A_i + 0$$

$$= A_i$$

$$Y_i = B_i + B_i' = 1$$

$$F = A_i \oplus 1 = A_i'$$

S_2	S_1	S_0	X	Y	Cin	F
0	0	0	A_i	0	0	A_i
0	0	1	A_i	B_i	0	$A_i + B_i$
0	1	0	A_i	B_i	0	$A_i + \bar{B}_i$
0	1	1	A_i	0	1	$A_i + 1$
1	0	0	$A_i B_i$	0	0	$A_i B_i$
1	0	1	A_i	B_i	0	$A_i \oplus B_i$
1	1	0	$A_i B_i$	0	0	$A_i + B_i$
1	1	1	A_i	1	0	A_i'

Table করা নাগর্যের
যথেষ্ট কর্তৃপক্ষ.

Q.18

a) $F = A + \bar{B}$

if $A = B$, that means $\bar{B} = \bar{A}$

$$so, A + \bar{A} = 01$$

$$so, F = 01$$

b). Count = 1 if $A + \bar{B} \geq 2^n$.

$$\Rightarrow A - B - 1 \geq 2^n \quad [\because \bar{B} = -B - 1]$$
$$\Rightarrow A - B + 2^n - 1 \geq 2^n \quad [\because -1 = all 1 = 2^n - 1]$$
$$\Rightarrow A \geq B + 1$$

Sub: All the Count = 1 if $F \geq 2^n$
equations:

Day	/ /
Time:	/ /
Date:	/ /

$$\textcircled{1} \quad F = A.$$

$$= A + 0 + 0.$$

So, Count = 0 always.

$$\textcircled{2} \quad F = A + 1.$$

\textcircled{3} Count = 1 if $F \geq 2^n$

$$\text{or, } A + 1 \geq 2^n$$

$$\text{or, } A \geq 2^n - 1.$$

$$\textcircled{3} \quad F = A + B.$$

$$\text{Count} = 1 \text{ if } A + B \geq 2^n.$$

$$\textcircled{4} \quad F = A + B + 1$$

$$\text{Count} = 1 \text{ if } A + B + 1 \geq 2^n$$

$$\Rightarrow A + B \geq 2^n - 1.$$

$$\textcircled{5} \quad F = A - B - 1$$

$$\text{Count} = 1 \text{ if } A - B - 1 \geq 2^n$$

$$\text{Here, } -B - 1 = \bar{B}$$

$$\Rightarrow -B + 2^n - 1 = \bar{B}$$

$$\text{So, } A + \bar{B} \geq 2^n.$$

$$\text{or, } A - B + 2^n - 1 \geq 2^n.$$

$$\text{or, } A \geq B + 1.$$

$$\textcircled{6} \quad F = A - B$$

$$\text{Count} = 1 \text{ if } A - B \geq 2^n$$

$$-B = \bar{B} + 1$$

$$\Rightarrow -B = -B - 1 + 1$$

$$\text{So, } A + \bar{B} + 1 \geq 2^n$$

$$\Rightarrow A - B - 1 + 1 \geq 2^n$$

$$\Rightarrow A - B + 2^n - 1 \geq 2^n$$

$$\Rightarrow A \geq B.$$

$$\textcircled{7} \quad F = A - 1$$

$$\text{Count} = 1 \text{ if } A - 1 \geq 2^n$$

$$\Rightarrow A + 2^n - 1 \geq 2^n$$

$$\Rightarrow A \geq 1.$$

$$\textcircled{8} \quad F = A \therefore \text{with Count} = 1.$$

$$\text{Here, } F = A + 1 - 1$$

$$= A + 1 + 2^n - 1$$

$$= A + 2^n.$$

So, always . Count = 1.

Next

(S)

Quiz-1 (Set-A)

a) Given $F = A - B - 1$ we know, $F \geq 2^n$ then $\text{Count} = 1$
if ~~Count = 1~~ then, $A + \bar{B} \geq 2^n$. $[\because \bar{B} = -B - 1]$

We know, $\bar{B} = -B - 1$

$$\Rightarrow \bar{B} = -B + (2^n - 1) \quad [\because \text{all } 1 = -1 = (2^n - 1)]$$

So, $A + \bar{B} \geq 2^n$

$$\Rightarrow A + 2^n - 1 - B \geq 2^n$$

$$\Rightarrow A - B - 1 \geq 0$$

$$\Rightarrow A - B \geq 1$$

$$\Rightarrow A \geq 1 + B$$

b) $F = A - B$.

if ~~Count = 1~~ then, $A + \bar{B} + 1 \geq 2^n$. $[\because F - B = \bar{B} + 1]$

$$\Rightarrow A - B + (2^n - 1) + 1 \geq 2^n$$

$$\Rightarrow A - B \geq 0$$

$$\Rightarrow A \geq B$$

c) $F = A - 1$

so, $A - 1 \geq 2^n$.

$$\Rightarrow A + 2^n - 1 \geq 2^n \quad [\because -1 = \text{all } 1 \text{ and all } 1 = 2^n - 1]$$

$$\Rightarrow A \geq 1$$

	1	0	1	0	1	0	A
1	1	0	1	0	1	0	
0	0	1	0	1	0	1	
0	0	0	0	0	0	0	
1	1	0	1	0	1	0	

$(F, 1, 0, 1, 0, 1, 0, 1) \in S$

$(\bar{F}, 0, 1, 0, 1, 0, 1, 0) \in S$

(A-12) 1-std. D.

d) $F = A$; $C_{out} = 1$

$$\text{So, } F = A - 1 + 1 = A + \text{all } 1 + 1$$

$$\text{So, } A + \text{all } 1 + 1 > 2^n$$

$$\Rightarrow A + 2^n - 1 + 1 > 2^n (A - 1) + 1 - 1 = A$$

 \Rightarrow

d) $F = A$; $C_{out} = 1$

$$\text{So, } F = A - 1 + 1$$

$$= A + \text{all } 1 + 1$$

$$= A + 2^n - 1 + 1$$

$$= A + 2^n$$

always $[C_{out}=1]$ $\leq 1 + A + 1$ (next $T=1$)

Max. n. n.


$$\textcircled{2} \quad F_1(A, B, C) = \sum(2, 4, 7)$$

$$= (A'B'C' + A'B'C + ABC)$$

$$= \{(A'B'C')'(AB'C)' \cdot (ABC)'\}$$

$$F_2(A, B, C) = \sum(0, 3) = \{(A'B'C')'(A'BC)\}'$$
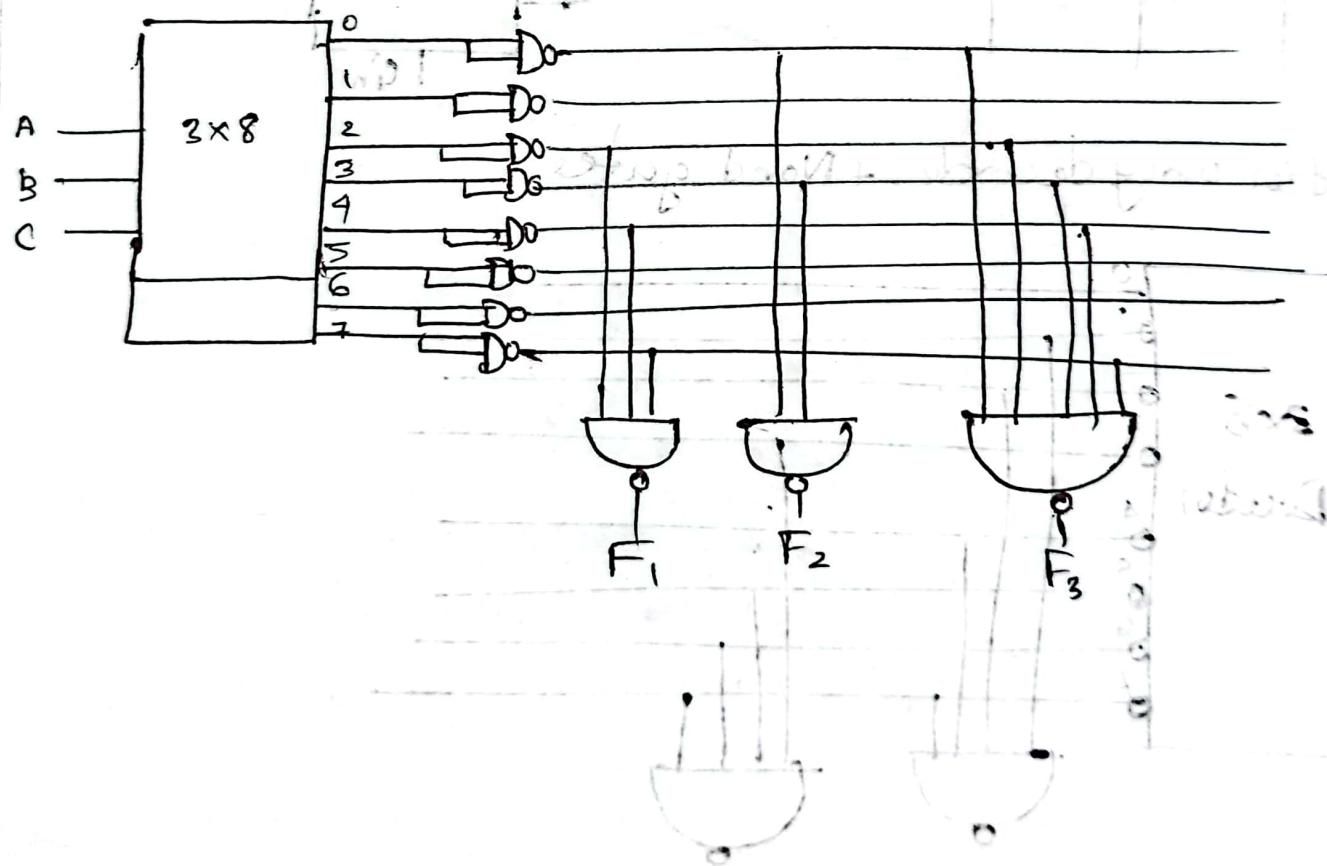
$$F_3(A, B, C) = \sum(0, 2, 3, 4, 7) = \{(A'B'C')'(A'BC) \cdot (AB'C)' \cdot (ABC)'\}$$



Set - B


1

S_2	S_1	S_0	F^n	X_i	Y_i	Z_i
0	0	0	$F = E, \text{Cout} = 1$	E	0	1
0	0	1	$E - F - 1 = E + F$	E	\bar{F}	0
0	1	0	$E + E + 1$	E	0	1
1	0	0	$\cancel{E} + F$	$\bar{E} + F$	0	0
1	1	0	$E \oplus F$	$E \oplus F$	0	0


$$X_i = S_2'E + S_2S_1'S_0(E+F) + S_2S_1S_0'(E \oplus F)$$

$$Y_i = S_2'S_1S_0\bar{F}$$

$$Z_i = S_2'S_0$$

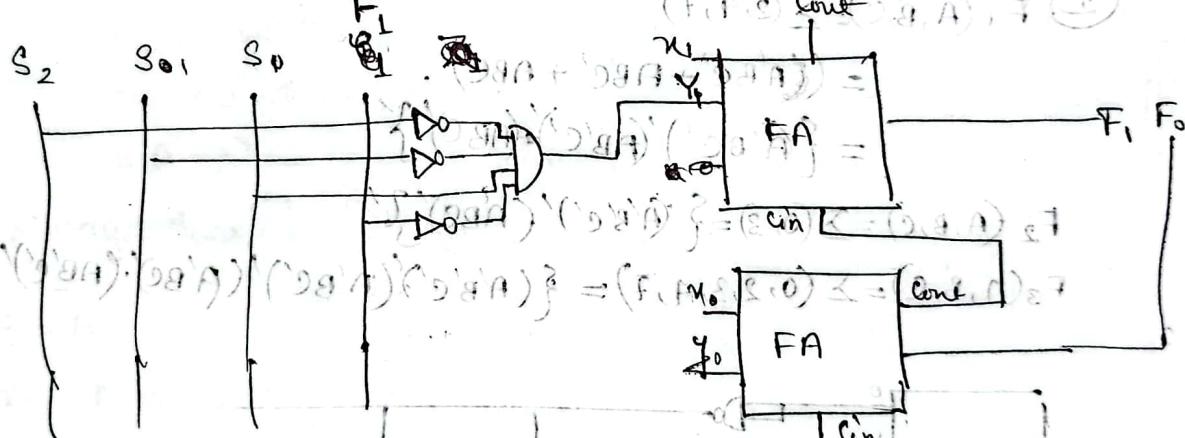

2 Full adder using decoder + Nand gates

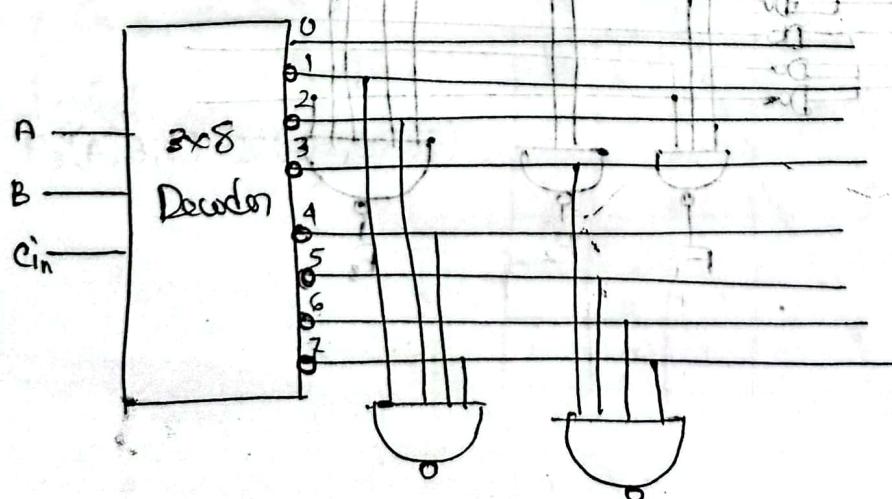

~~Q1~~ Quiz-1 (A) Set C.

$$\textcircled{1} \quad x_i = A_i + (S_2' S_1' S_0)' A_i B_i + S_2 S_1' S_0' B_i$$

$$y_i = S_2 S_1 S_0 B_i + S_0 B_i' (S_2' S_1' S_0')$$

$$z_i = S_2' C_{in}$$

$$\textcircled{i} \quad (S_2, S_1, S_0, C_{in}) = (0, 0, 0, 0) \quad [\text{Given}]$$

~~$$z_i = C_{in} = 0$$~~

$$x_i = A_i + (1, 1, 1)' A_i B_i + 0, 1, 0, B_i$$

$$= A_i$$

$$y_i = 0 + 0, B_i' (0, 0, 0)'$$

$$= 0$$

$$F = A_i$$

$$\textcircled{ii} \quad (S_2, S_1, S_0, C_{in}) = (1, 0, 0, 0)$$

$$z_i = 0 \quad [\text{Logical}]$$

$$x_i = A_i + (0, 1, 1)' A_i B_i + 1, 1, 1, B_i$$

$$= A_i + A_i B_i + B_i$$

$$= A_i (B_i + 1) + B_i$$

$$= A_i + B_i \quad [\text{OR - Logical}]$$

~~$$y_i = 1, 0, 0, B_i + 0, B_i' (1, 0, 1)'$$~~

$$= 0$$

$$F = A_i + B_i$$

$$= A_i \vee B_i$$

$$\textcircled{iii} \quad (S_2, S_1, S_0, C_{in}) = (0, 0, 1, 1)$$

$$z_i = C_{in} \quad [\text{Arithmetic}]$$

$$x_i = A_i + (1, 1, 0)' A_i B_i + (0, 1, 0) B_i$$

$$= A_i + A_i B_i + 0$$

$$= A_i (1 + B_i) = A_i$$

$$y_i = 0, 0, 1, B_i + 1, B_i' (0, 0, 0)'$$

$$= 0 + B_i' = B_i'$$

$$F = A + \overline{B}_i$$

$$\textcircled{iv} \quad (S_2, S_1, S_0, C_{in}) = (1, 1, 1, 1)$$

$$z_i = 0 \quad [\text{Arithmetic, since } C_{in} = 1]$$

$$x_i = A_i + (0)' A_i B_i + (1, 0, 0) B_i$$

$$= A_i + A_i B_i + 0$$

$$= A_i$$

$$y_i = 1, 1, 1, B_i + 1, B_i' (1, 1, 0)'$$

$$= B_i + B_i' = 1$$


$$F = A_i + 1$$

Q) 4 bit comparator.

$A_4 B_4$	$A_3 B_3$	$A_2 B_2$	$A_1 B_1$	$F \rightarrow (A = B)$
$A_4 > B_4$				0
$A_4 < B_4$				0
$A_4 = B_4$	$A_3 > B_3$			0
$A_4 = B_4$	$A_3 < B_3$			0
$A_4 = B_4$	=	$A_2 > B_2$		0
$A_4 = B_4$	=	$A_2 < B_2$		0
$A_4 = B_4$	=	$A_1 > B_1$		0
$A_4 = B_4$	=	$A_1 < B_1$		0
$A_4 = B_4$	=	=		1
$A_4 \neq B_4$	/	/		
$A_4 \neq B_4$	/	/		

$$\text{So, } F = (A_4 \oplus B_4) (A_3 \oplus B_3) (A_2 \oplus B_2) (A_1 \oplus B_1).$$


Design.

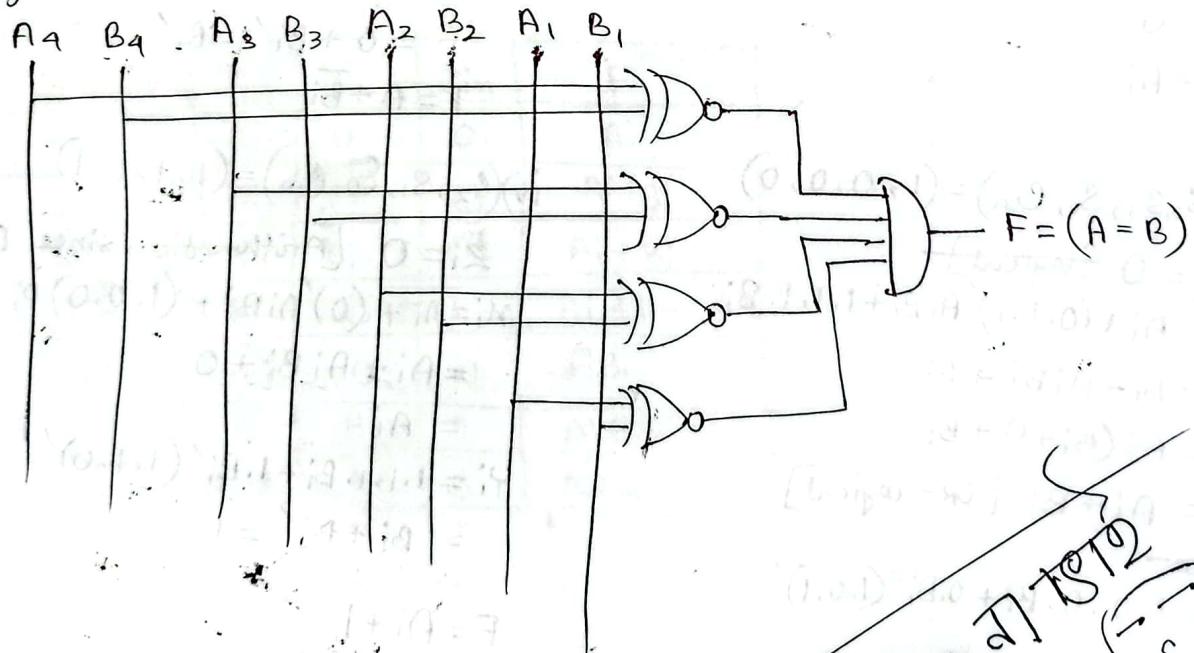

extra Suse 27 TSP
take Risk

Assignment 1

① 4x4 RAM:

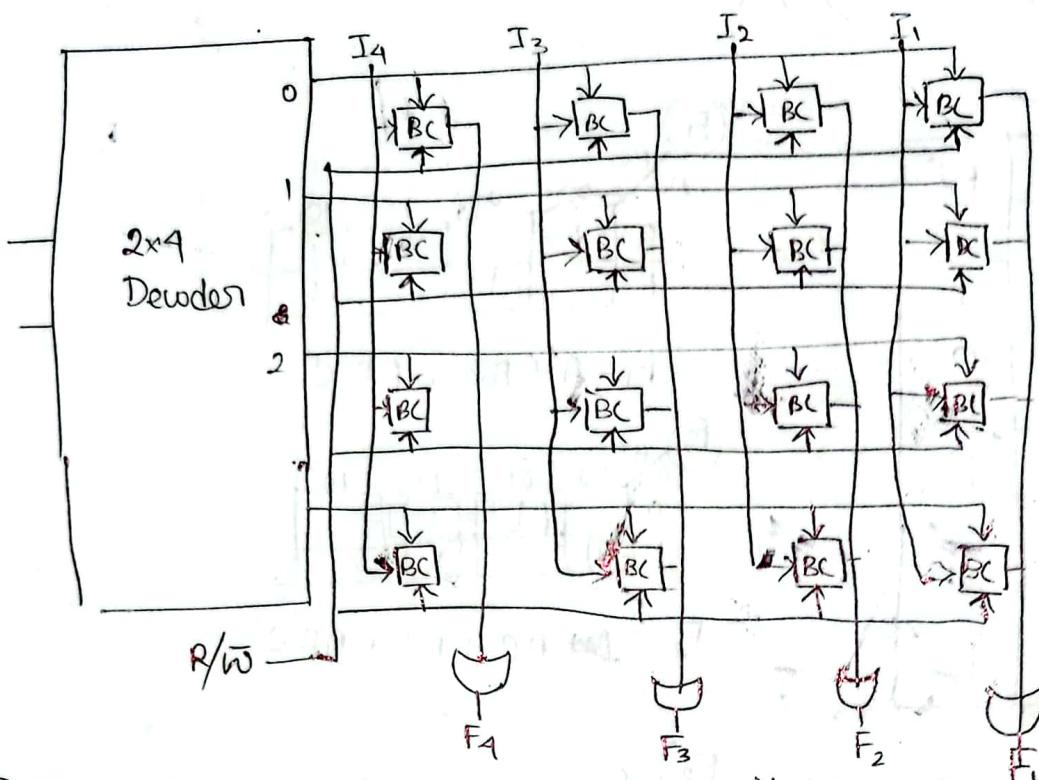

No, 'D11' cannot be read/write from this RAM as it has 3 words and the RAM drawn is 4x4 RAM. It will read and write data with 4 bits.

① The printer that is ready and available will start printing first for first two parallel transfer methods.

In case of Simple I/O, each printer have a dedicated line where the computer places data and any printer that is ready receives it first.

In case of Simple Strobe I/O, computer sends a strobe with data and the first printer to receive it starts first.

Again for Single-Handshake I/O, computer sends ~~data~~ request to ~~a printer~~ each printer in sequence. The printer that responds with an acknowledgement first gets to receive the data. The prioritize device is the one who handshakes first.

Lastly for double Handshake I/O, the printer who responds first gets the data and starts printing first. It also ensures that the printer received the command precisely and is on its way to output.


Thus first two methods do not have any prioritization whereas the last two do have and which printer gets priority depends on its responsiveness.

$$\textcircled{2} \quad F_1(A, B, C) = \prod(1, 3, 4, 7) = \sum(0, 2, 5, 6)$$


$$F_2(A, B, C) = \prod(0, 2, 5, 6) = \sum(1, 3, 4, 7).$$

TT:


A	B	C	F1	F2
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

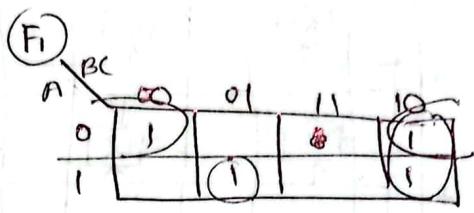

$$F_1 = A' + BC' + AB'C$$

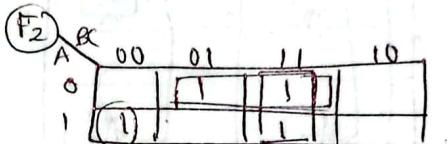

$$F_2 = A'C + BC + AB'C'$$

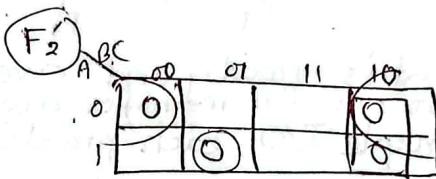


$$F_2' = A' + BC' + ABC$$

let's take F_1 and F_2'

Program table:


	A	B	C	F1	F2'
A'	1	0	-	1	1
BC'	2	-	1	0	1
AB'C	3	1	0	1	1

Circuit

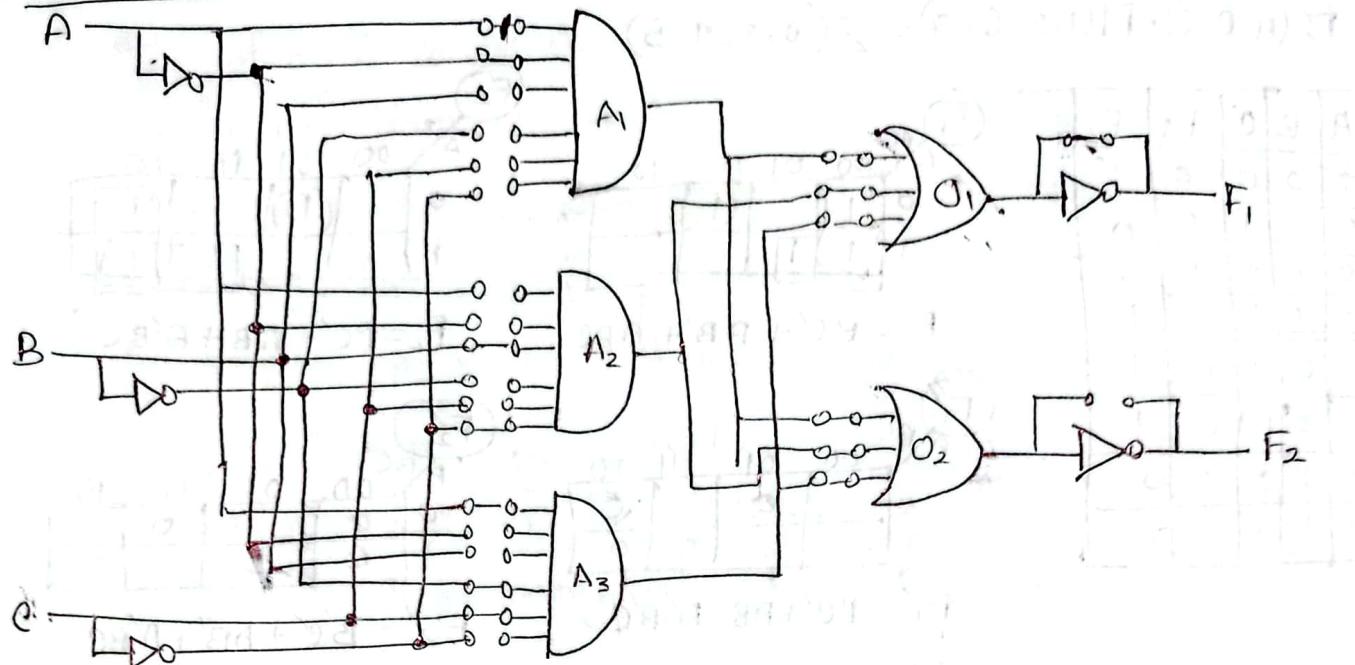

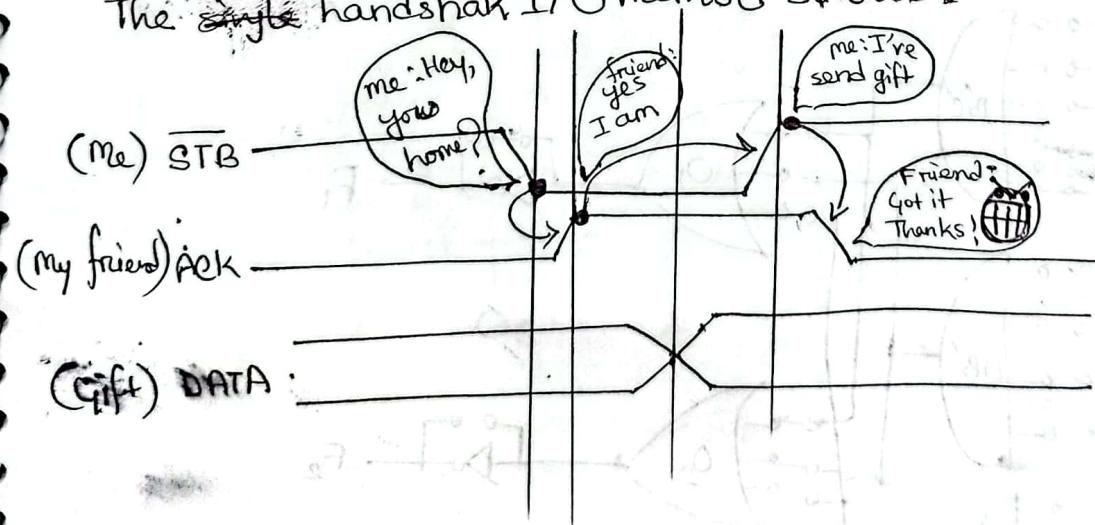- (3) According to single handshake I/O, I ~~wouldn't send the gift~~ as I ~~had~~
- (3) According to single or double handshake I/O of parallel transfer methods calling my friend ~~was~~ is similar to sending a strobe to ensure that my friend is ready to receive. As he did not respond I would not send the gifts.. I would have send if he was available.

The ~~single~~ double handshake I/O method shows:




(4)

$$F_1(A, B, C) = \prod(0, 3, 4, 5) = \sum(1, 2, 6, 7)$$


$$F_2(A, B, C) = \prod(1, 2, 6, 7) = \sum(0, 3, 4, 5)$$

T.T.:


A	B	C	F_1	F_2
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

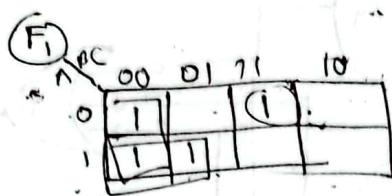


$$F_1 = B'C' + AB' + A'BC$$

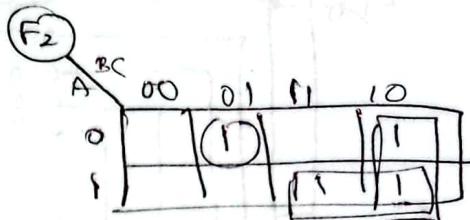

$$F_2 = BC' + AB + A'B'C$$

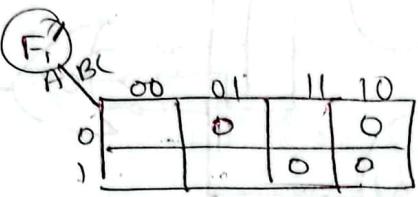

$$F_1' = BC' + AB + A'B'C$$

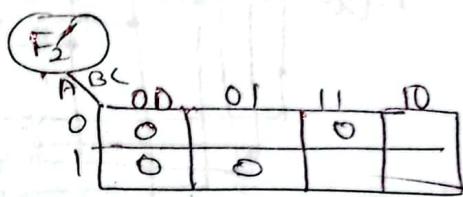


$$F_2' = B'C' + AB' + A'BC$$

Let's take, F_1 and F_1'

Program table:


Program Terms	Inputs			Outputs	
	A	B	C	F_1	F_2
$B'C'$	1	-	0	0	1
AB'	2	1	0	-	1
$A'BC$	3	0	1	1	1

Circuit:

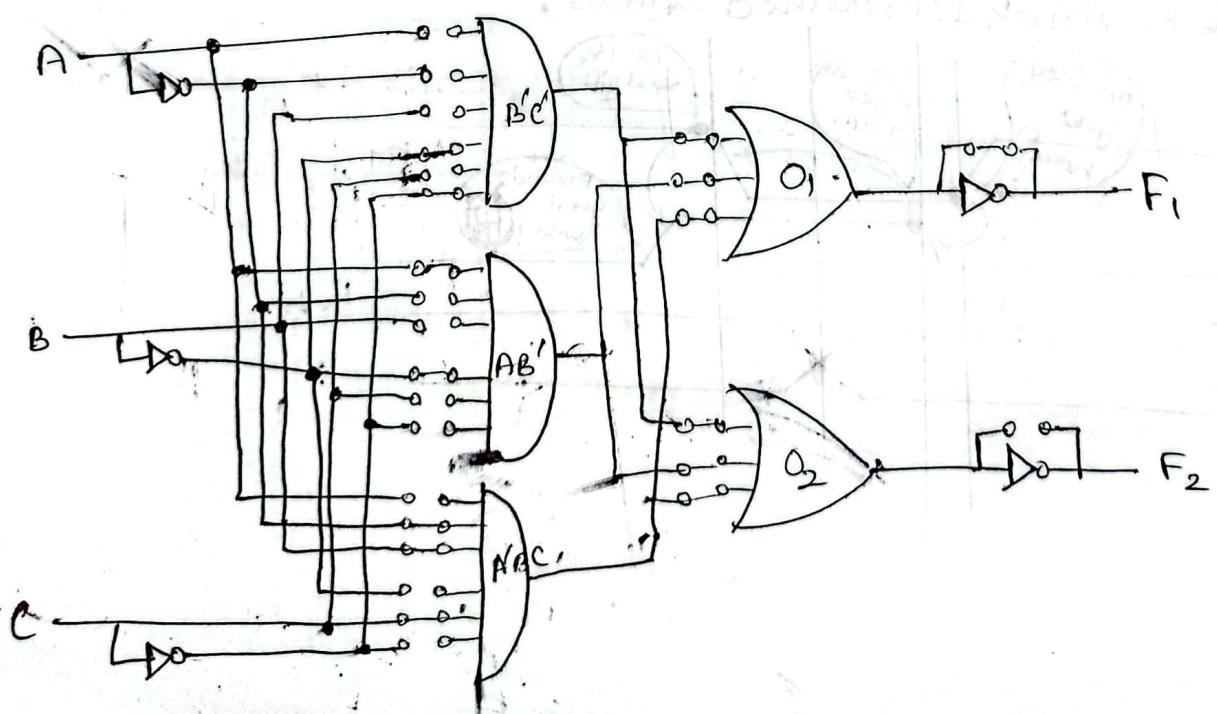

- ⑤ Double handshaker I/O is the best.
- First of all it sends strobe and seeks acknowledgement of the receiver if its ready or available to receive or not.
- Then again after sending data, sender sends another strobe claim informing they sent data.
- The receiver sends the 2nd ack letting sender know that the data is successfully received.
- The communication btw sender receiver is good here.
- Thus it is best among all. [Fig: 3 ~~mark~~ mark ~~একাধিক~~ একাধিক]

⑥ 4x6 RAM

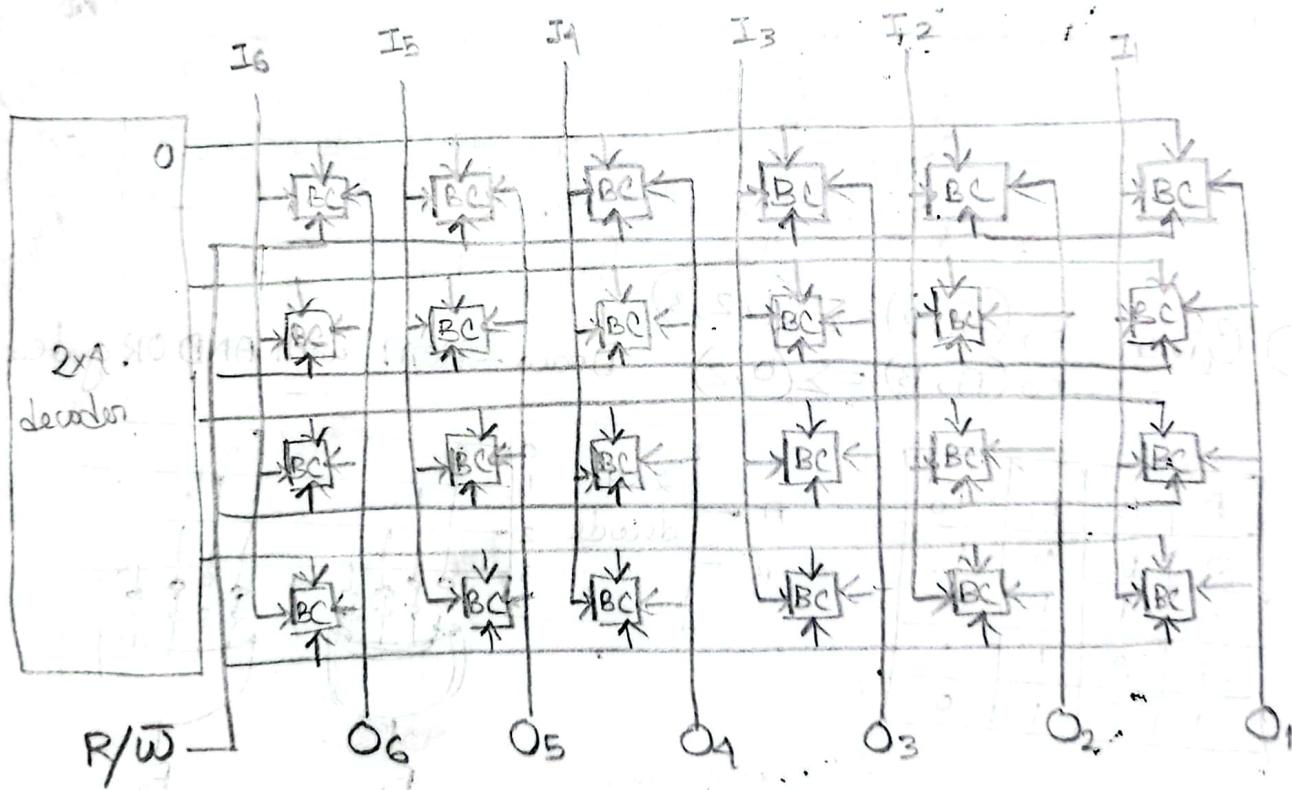

Lecture - Practice: ~~2048x8 ROM~~ 2048 bit ROM - word size = 8 words.


$$2048/8 = 256$$

So, 256×8 ROM or $2^8 \times 8$ ROM.

Here, $n=8$, $m=8$. [$\because 2^n \times m$ ROM]


$$\text{Range} = (0000\ 0000 - 1111\ 1111)_2 \text{ or } (0-255)_{10}$$

Design: Logic diagram

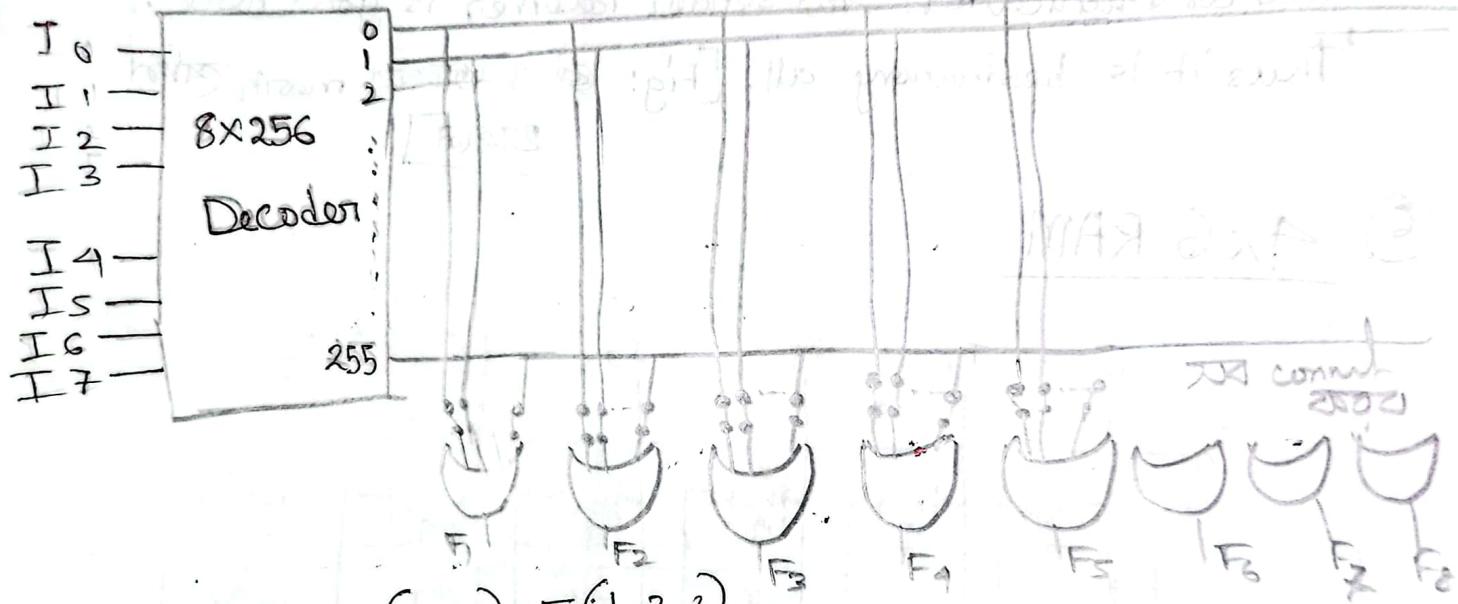


Given $F_1(A, B) = \sum(1, 2, 3)$
 $F_0(A, B) = \sum(0, 2)$ Draw - ROM with AND OR gates

A	B	F_1	F_0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

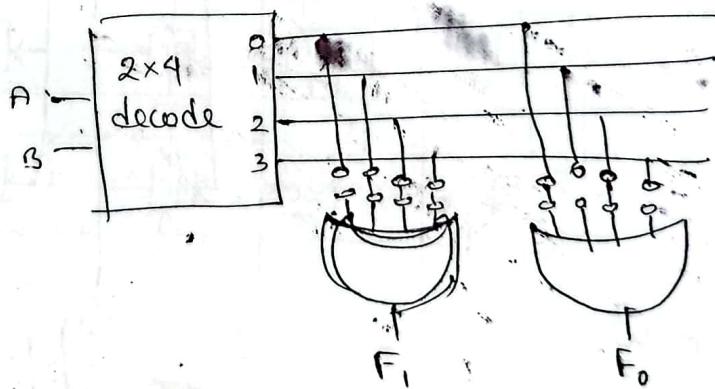


With AND OR invert-gate then,

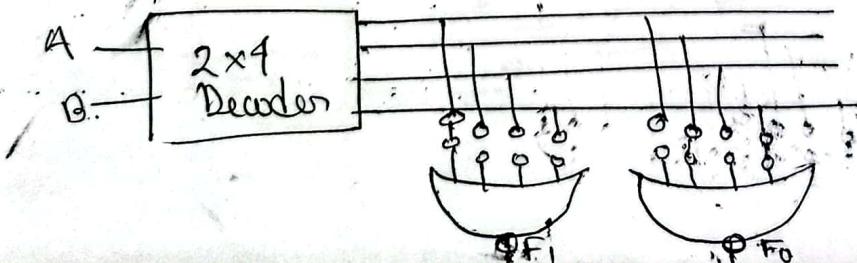

Assignment-2

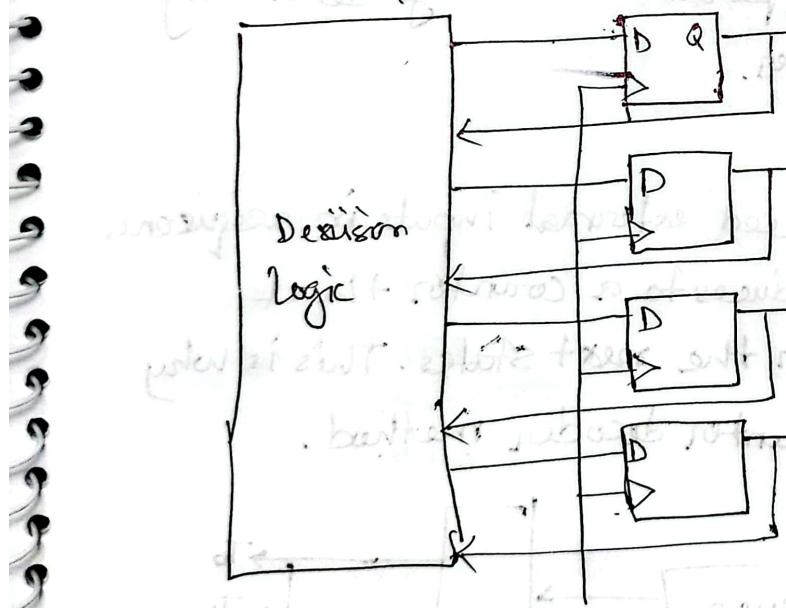
- ① When external inputs are absent the One ff per state method reduces to a ring counter controller with a straight single bit shift register.



Here, as external inputs are not present the control sequence repeats over and over again which makes it a ring counter.


Only one ff set at any time and all other are cleared and each ff represents a state. Transition from present to next state is a function of T_i which is 1 and certain input conditions and each ff connected to the data processing section.

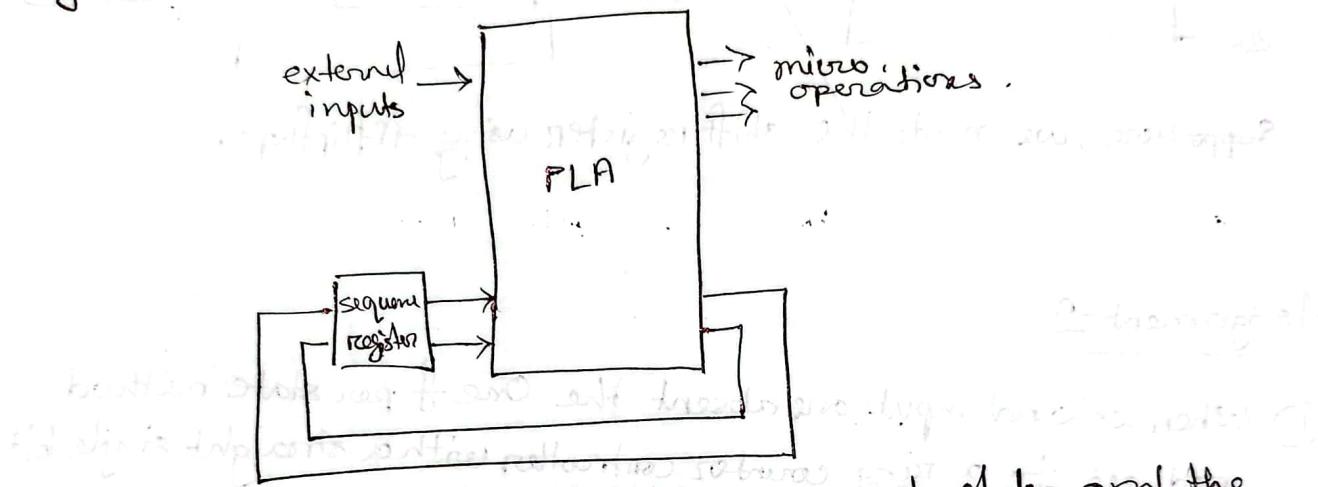② We can improve "Sequence register and decoder" by implementing a PLA instead of combinational circuits and reducing numbers of ICs and wires. A sequence register and decoder consists of decoder and decision logic that is replaced by PLA.



external sequence register establishes present state and the outputs of PLA initiates micro operation including determining next states of sequence register.

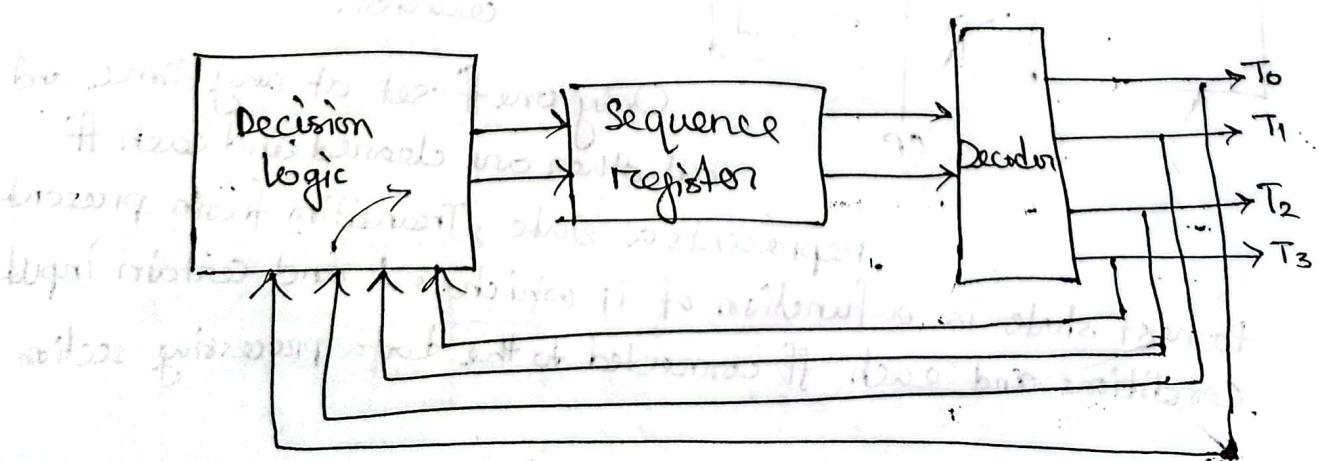If the control circuit does not need external inputs in sequence register and decoder that it reduces to a counter that continuously sequences through the next states. This is why it is sometimes called a counter decoder method.



SAP2 codes — subroutine times maths:

From PDF:

① time = $1\mu s$ or $f = \frac{1}{t}$ (frequency $\rightarrow 1MHz$)

Code: MVI C, 96H

AGAIN: DCR C

JNZ AGAIN

NOP

RET.

Solution:— 96H = 70(Dec).

→ [formula → loops × tstates × time]

MVI C : $1 \times 7 \times 1\mu s$

DCR C : $70 \times 4 \times 1$

JNZ : $69 \times 10 \times 1$

no JNZ : $1 \times 7 \times 1$

NOP : $1 \times 4 \times 1$

RET : $1 \times 10 \times 1$

$$\text{Total} = 1 + 70 + 69 + 1 + 4 + 10 = 998 \mu s \approx 1ms$$

Code: MVI B, 0AH

Loop1: MVI C, 47H

Loop2: DCR C

JNZ Loop2

DCR B

End = JNZ End

RET

Solution:—

inner loop
start
end

MVI C : ~~$71 \times 7 \times 1\mu s$~~

DCR C : ~~$71 \times 4 \times 1\mu s$~~

JNZ : ~~$70 \times 10 \times 1$~~

no JNZ : ~~$1 \times 7 \times 1$~~

—

991 ~~μs~~

CB21 27/09

Tstates

MVI

MVI → 7

DCR

DCR → 4

JNZ

JNZ → 10/7

RET

RET → 10

NOP

NOP → 4

Here,

0AH = 10D

47H = 71D

শেষ লুপ কোড আসুন

MVI C : $10 \times 7 \times 1 \mu s$

loop 2 : 10×991

DCR B : $10 \times 4 \times 1$

JNZ : $9 \times 10 \times 1$

no JNZ : $1 \times 7 \times 1$

MVI B : $1 \times 7 \times 1 \mu s$

10124 μs

RET : $1 \times 10 \times 1 \mu s + (10124 \mu s)$

delay time = $10134 \mu s$ (Ans)

Fall-2 2 - 20 code :

MVI C, 05H

START: MVI B, 65H

ODD: MVI A, 32H

EVEN: DCR A

JNZ EVEN

DCR B

JNZ ODD

DCR C

JNZ START

RET.

Solution :-

(inner loop তারে)

DCR A : $50 \times 4 \times 0.5 \mu s$

JNZ EVEN : $9 \times 10 \times 0.5$

no JNZ : $1 \times 7 \times 0.5$

348.5 MS

Here,

05H = 5D

65H = 101D

32H = 50D

MVI A : $101 \times 7 \times 0.5$

EVEN : 101×348.5

DCR B : $101 \times 4 \times 0.5$

JNZ ODD : $100 \times 10 \times 0.5$

no JNZ : $1 \times 7 \times 0.5$

36257.5

MVI B: $5 \times 7 \times 0.5 \mu s$ + Loop odd: 5×36257.5 .

→ start loop

DCR C: $5 \times 4 \times 0.5 \mu s$

JNZ START: $4 \times 10 \times 0.5$.

No. JNZ: $1 \times 7 \times 0.5$

MVI C: $1 \times 7 \times 0.5$

RET ! $1 \times 10 \times 0.5$

1818347 μs .

Fall-22

2/b: Handshaking sequence:

1. READY bit (bit 0, port 2) goes high.
2. Input the data in port 1 to CPU.
3. ACKNOWLEDGE bit (bit 7, port 4) goes high to reset READY bit.
4. Reset the ACKNOWLEDGE bit

During execution, all T states do nothing when we give NOP or No operation. It is used to waste time or delay data processing.

It takes 4 T states to fetch NOP.

So if we put NOP in a loop that executes 100 times, a delay of 400T states is created.

Quiz-4

Set - A

② Instruction cycle for ADD 9H

$$T_1 : E_P \bar{L}_m$$

$$T_2 : C_P$$

$$T_3 : \bar{C}E \quad \cancel{E_I} \bar{L}_I$$

$$T_4 : \bar{L}_m \bar{E}_I$$

$$T_5 : \bar{C}E \bar{L}_B$$

$$T_6 : \bar{L}_A E_U$$

Set B

② Instruction cycle for LDA 7H

$$T_1 : E_P \bar{L}_m$$

$$T_2 : C_P$$

$$T_3 : \bar{C}E, \bar{L}_I$$

$$T_4 : \bar{L}_m \bar{E}_I$$

$$T_5 : \bar{C}E \quad \cancel{B} \bar{L}_A$$

$$T_6 : X$$

Set - C

② Microinstructions for ADD.

$$T_1 : MAR \leftarrow PC$$

$$T_2 : PC \leftarrow PC - 1$$

$$T_3 : IR \leftarrow RAM[MAR]$$

$$T_4 : MAR \leftarrow IR(3...0)$$

$$T_5 : B \leftarrow RAM[MAR]$$

$$T_6 : ACC \leftarrow ACC + B$$

Control Words for Machine Cycle's ADD

$T_1, CON = C_P E_P \bar{L}_m \bar{C}E$	$\bar{E}_I \bar{E}_I \bar{L}_A E_A$	$\cancel{S}_U E_U \bar{L}_B \bar{L}_O$	$0011 = 5E3$
$= 0101$	1110	0011	$= BE3$
$T_2, CON = 1011$	11010	0011	$= 273$
$T_3, CON = 0010$	0110	0011	$= 1A3$
$T_4, CON = 0001$	1010	0001	$= 2E1$
$T_5, CON = 0010$	1110	0111	$= 3C7$
$T_6, CON = 0011$	1100	0111	

Set-D

② Micro operations of LDA.

T₁: MAR \leftarrow PC

T₂: PC \leftarrow PC-1

T₃: IR \leftarrow RAM

T₄: MAR \leftarrow IR

T₅: ACC \leftarrow RAM.

T₆: X

Control words for LDA:

CON = CP EP \bar{E}_m \bar{CE}

\bar{E}_I \bar{E}_I \bar{L}_A E_A

~~SU~~ E_U \bar{L}_B \bar{L}_o

~~0011~~ = 5 E 3

~~0011~~ = 6 BE 3

~~0011~~ = 2 B 3

~~T₁~~ = 0 1 0 1

1 1 1 0

~~0011~~ = 5 E 3

~~T₂~~ = 1 0 1 1

1 1 1 0

~~0011~~ = 6 BE 3

~~T₃~~ = 0 0 1 0

0 1 1 0

~~0011~~ = 2 B 3

~~T₄~~ = 0 0 0 1

1 0 1 0

~~0011~~ = 1 A 3

~~T₅~~ = 0 0 1 0

1 1 0 0

~~0011~~ = 2 C 3

~~T₆~~ = 0 0 1 1

1 1 1 0

~~0011~~ = 3 E 3

Set-E

② Timing diagram for LDA GH:

T₁ = EP \bar{L}_m


T₄ = \bar{L}_m \bar{E}_I

T₂ = CP

T₅ = \bar{CE} \bar{L}_A

T₃ = \bar{CE} \bar{L}_I

T₆ = X

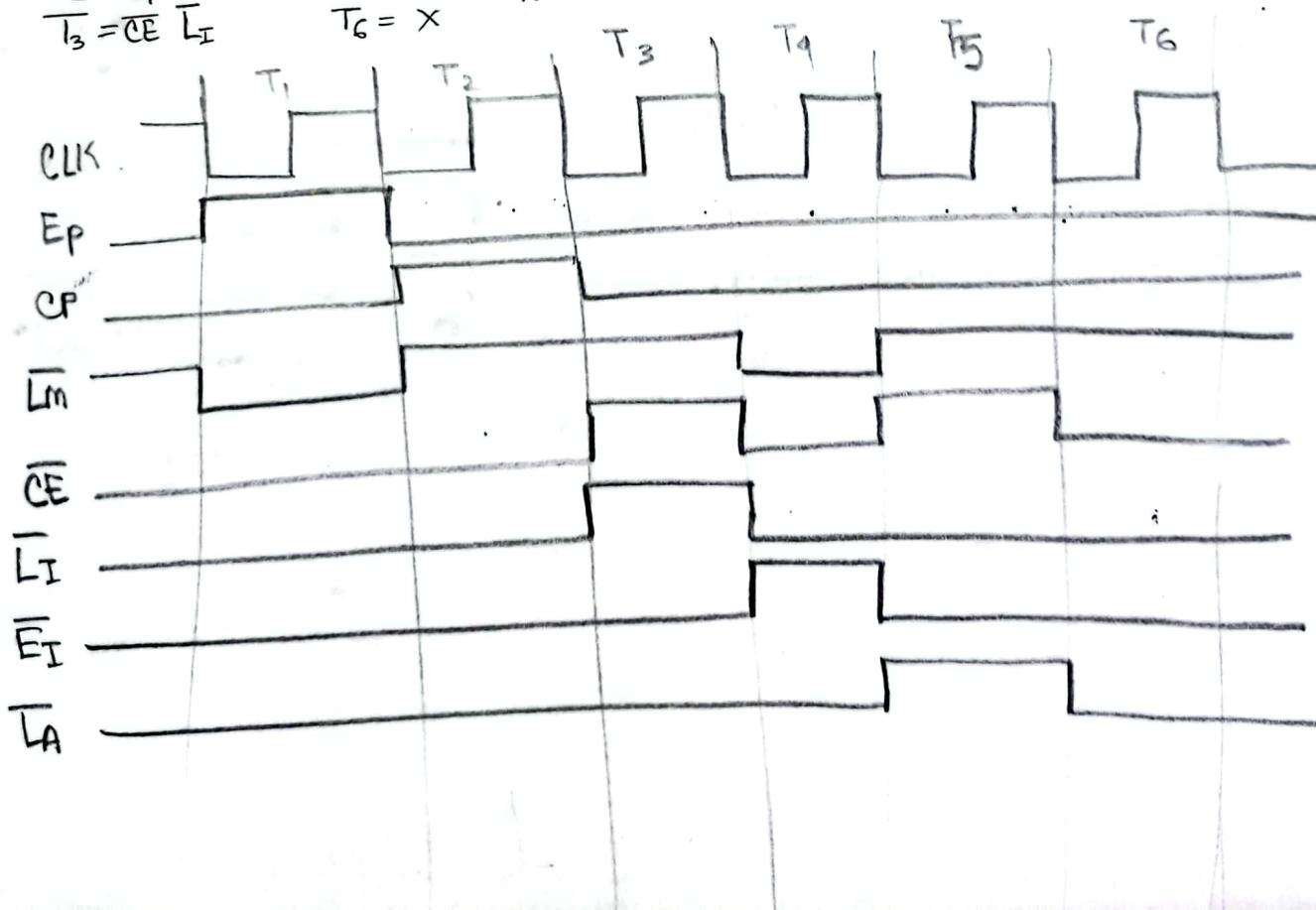

Sdt - F

② Timing diagram for 8085H.

T₁: E_p \bar{E}_m

T₄: \bar{E}_m E_I

T₂: C_P

T₅: $\bar{C}E$ \bar{E}_B

T₃: $\bar{C}E$ \bar{E}_I

T₆: \bar{E}_A E_U S_U



Quiz-2 Set C :- $2048/16 = 128$; range = $(0000\ 000 - 1111\ 111)_2$ or $(0-127)_{10}$.

01	$\rightarrow +4$
10	$\rightarrow -4$

Set-A

① Design বলা (UV ক্রম) Given, -17×23 .

$$x = -17 = 01111$$

$$y = 23 = 10111$$


$$-y = -23 = 01001$$

x	y	x	$(x-1)$	steps
000000	000000	011111	0	1.
$(-y) + 01001$		001111	1	
$\overline{+ 01001}$				
$\overline{RS \rightarrow 001\ 00}$	$100\ 00$			
$(+) 0$				2.
$001\ 00$				
$RS \rightarrow 000100$	010000	000011	1	3
$+ 0$				
000010				
$RS \rightarrow 000010$	001000	000001	1	4
$+ 0$				
000001				
$RS \rightarrow 000000$	100010	000000	1	5
$(+y) + 01111$				
$\overline{+ 01111}$				

So, RS $\rightarrow 0011111001$ = Final result. (মিল না 😞)

Set-B

State diagram:

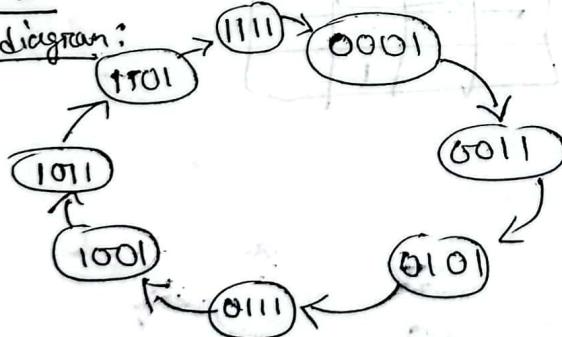

State table:

	1111	0001	0011	0101	0111	1001	1011
1111	0001	0011	0101	0111	1001	1011	1111

State Table:

00 - 0X
01 - 1X
10 - X0
11 - XX

PS				NS				J _A				K _A				J _B				K _B				J _C				K _C				J _D				K _D			
A	B	C	D	A	B	C	D	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D																								
0	0	0	1	0	0	1	1	0	X	0	X	1	X	1	X	0																							
0	0	1	1	0	1	0	1	0	X	1	X	X	1	X	0																								
0	1	0	1	0	1	1	1	1	X	X	X	0	1	X	X	0																							
1	0	1	1	1	0	0	1	1	X	X	1	X	1	X	1	X	0																						
1	0	0	1	1	0	1	1	1	X	0	0	X	1	X	X	0																							
1	0	1	1	1	1	1	0	0	X	0	1	X	X	1	X	1	X	1	X	1	X	1	X	0															
1	1	0	1	1	1	1	1	1	X	0	X	0	1	X	X	0																							
1	1	1	0	1	0	0	0	0	X	1	X	1	X	1	X	1	X	1	X	1	X	1	X	0															

JA	CD	AB
00	00	01
01	X	X
11	X	X
10		

$$J_A = A'B + CD.$$

JA	CD	AB
00	00	01
01		
11	X	X
10	X	X

$$J_A = AD + BC'D.$$

KA				
X	X	1	X	X
X	X	X	X	
X	X	X	X	
				1

KA				
X	X	X		
X	X	X		
X	X	X		
				1

$$K_A =$$

Set D $F_1 = abc + \bar{a}b + a$

$$= abc + \bar{a}bc + \bar{a}\bar{b}\bar{c} + ab + \bar{a}\bar{b}$$


$$= abc + \bar{a}bc + \bar{a}\bar{b}\bar{c} + ab\bar{c} + a\bar{b}\bar{c} + a\bar{b}c$$

$$= \Sigma(7, 3, 2, 6, 5)$$


$$F_2 = \Sigma(2)$$

$$F_3 = \Sigma(\bar{a}cb + \bar{a}c\bar{b}) = \Sigma(3, 2)$$

a	b	c	F_1	F_2	F_3
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	1	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	0	0

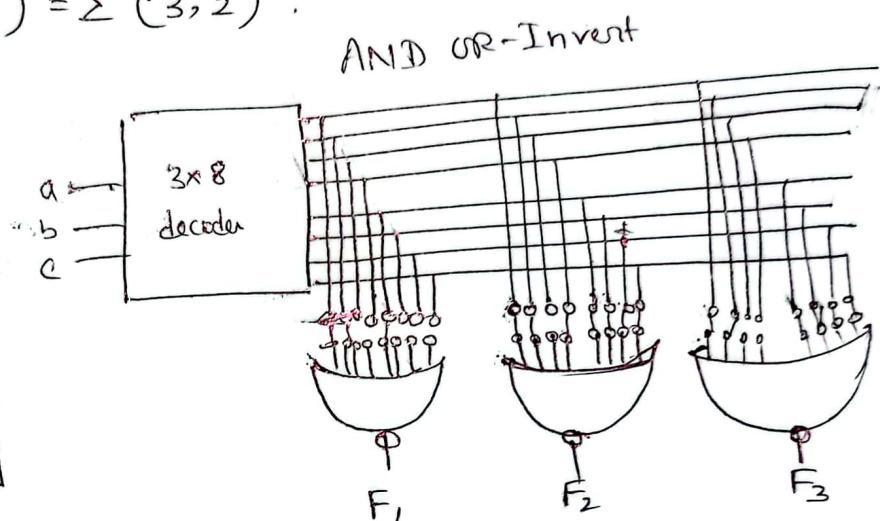

Set - F

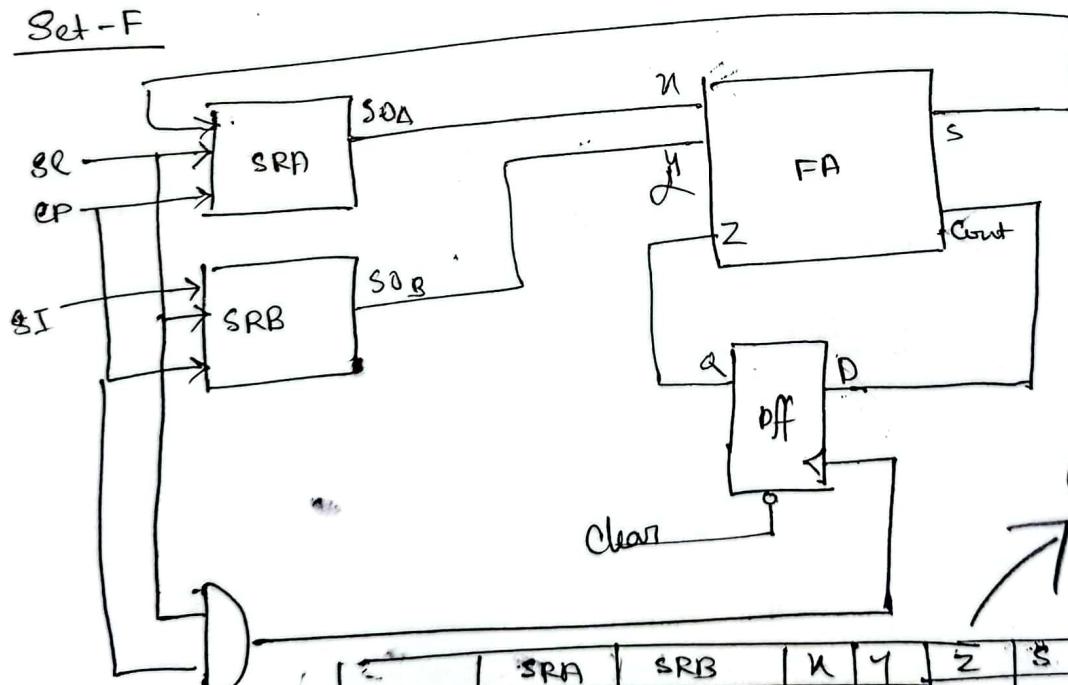

explain
कैसे यहाँ परिवर्तन

	SRA	SRB	Y	Z	S	C
	111	101	0	0	0	0
	011	10	1	1	0	0
	001	1	1	0	1	0
	100	x	1	1	1	1

$S_0, SRA = 100$ and CarryOut = 1.