

1@ It states that every algebraic expression deducible from the postulates of Boolean algebra remains valid if the operators & identity elements are interchanged. For example: $E = (A \cdot S \cdot R) + (A \cdot S \cdot \bar{R})$
 if $A + \bar{A} = 1$ is true then $A \cdot \bar{A} = 0$ is also true

1.B

$$(\overline{ABC})(A+C)(A+\bar{C})$$

$$= (\overline{ABC})(A+CC) \quad [\text{or distributed law}]$$

$$= (\overline{ABC}) \cdot (A+0) \quad [C\bar{C}=0]$$

$$= (\overline{ABC}) \cdot A \quad [A+0=A]$$

$$= (A + \bar{B} + \bar{C}) \cdot A \quad [\text{DeMorgan law}]$$

$$= A \cdot \bar{A} + A \cdot \bar{B} + A \cdot \bar{C} \quad [\text{distributed law}]$$

$$= A\bar{B} + A\bar{C} \quad [A \cdot \bar{A} = 0]$$

* Determine the single error correcting code (Hamming code) for '101110110'

Soln: The no of data bits in the message, $n=9$. we can obtain the required no of parity bits (P) from the following formula: $2^P \geq n+p+1$

If $P=4$, $2^3 \geq 9+3+1$ (false); if $P=4$, $2^4 \geq 9+4+1$ (true)

So, $P=4$, we have to sent total $n+p=9+4=13$ bit message.

Bit position	1	2	3	4	5	6	7	8	9	10	11	12	13
Values	P ₄	P ₃	P ₂	P ₁	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	M

To find P₁, P₂, P₃, P₄ we have to X-OR the binary values of bit positions holding '1's

3 0 0 1 1
6 0 1 1 0
7 0 1 1 1
9 1 0 0 1
11 1 0 1 1
12 1 1 0 0

X-OR 0 0 0 0
P₄ P₃ P₂ P₁

Sending message code will be: 0011011110110

Receiving End: If there is no error, the receiver will get: 0011011110110

Verification:

Bit position	1	2	3	4	5	6	7	8	9	10	11	12	13
Values	0	0	1	1	0	1	1	1	1	1	0	1	1

Binary values of the bit position holding '1's:

3 0 0 1 1
4 0 1 0 0
6 0 1 1 0
7 0 1 1 1
8 1 0 0 0
9 1 0 0 1
11 1 0 1 1
12 1 1 0 0

X-OR 0 0 0 0

So, there is no error.

2. @

Given, $F(A, B, C, D) = \Sigma (1, 3, 5, 7, 9, 15)$
 $= \Sigma (0001, 0011, 0101, 0111, 1001, 1111)$

And, $d(A, B, C, D) = \Sigma (4, 6, 12, 13)$

$= \Sigma (0100, 0110, 1100, 1101)$ $\perp = \bar{B} + A$

AB	CD	00	01	11	10
00					
01	X	1	1		
10	X	X	1		
10		1			

$$F = C'D + A'D + BD$$

$$[0 = \bar{5} \circ (\bar{6} + A) \cdot (\bar{9} \bar{8} A)]$$

$$[0 = \bar{5} \circ (\bar{6} + A) \cdot (\bar{9} \bar{8} A) =$$

$$[\bar{A} = \bar{0} + A] \quad A \cdot \bar{(\bar{9} \bar{8} A)} =$$

$$[\bar{A} = \bar{0} + A] \quad A \cdot (\bar{5} + \bar{8} + \bar{A}) =$$

$$[\bar{A} = \bar{0} \cdot A] \quad \bar{5} A + \bar{8} A + \bar{A} \cdot A =$$

$$[0 = \bar{A} \cdot A] \quad \bar{5} A + \bar{8} A =$$

(2)

(b) Simplify the following Boolean function F by using the Quine-McCluskey method.

$$F(w, x, y, z) = \sum(0, 1, 2, 8, 10, 11, 14, 15)$$

$$\Rightarrow F(w, x, y, z) = \sum(0000, 0001, 0010, 1000, 1010, 1011, 1110, 1111)$$

Determination of prime implicants:

Column I	Column II	Column III
Group 0 0 0 0 0 ✓	0,1 0 0 0 - 0,2 0 0 - 0 ✓ 0,8 - 0 0 0 ✓	0,2,8,10 - 0 - 0 0,8,2,10 - 0 - 0
Group 1 1 0 0 0 1 ✓ 2 0 0 1 0 ✓ 8 1 0 0 0 ✓	2,10 . - 0 1 0 ✓ 8,10 1 0 - 0 ✓	
Group 2 1 0 1 0 ✓	10,11 1 0 1 - ✓ 10,14 1 - 1 0 ✓	10,11,14,15 1 - 1 - 10,14,11,15 + 1 1 2
Group 3 1 1 0 1 1 ✓ 14 1 1 1 0 ✓	11,15 1 - 1 1 ✓ 14,15 1 1 1 - ✓	
Group 4 1 5 1 1 1 1 ✓		

selection of prime implicants

PIs	w x y z	minterms						
		0	1	2	8	10	11	14
0, 2, 8, 10	- 0 - 0	x'z'2'	x		⊗	⊗	x	⊗
10, 11, 14 + 15	1 - 1 -	wy				x	⊗	⊗
0, 1	0 0 0 -	w'x'y'	x	⊗				

$$F = x'z' + wy + w'x'y'$$

checking:


	w'x'	w'x	wx	wx'
yz	00	01	11	10
y'z	01	1		
yz'	11		1	1
y'z'	10	1	1	1

$$F = wy + y'z'x' + w'x'y'$$

3. @


Decimal value	Binary Sum					Required BCD Sum				
	Cy	S ₃	S ₂	S ₁	S ₀	Cy	S ₃	S ₂	S ₁	S ₀
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1
					X					

Q. 8

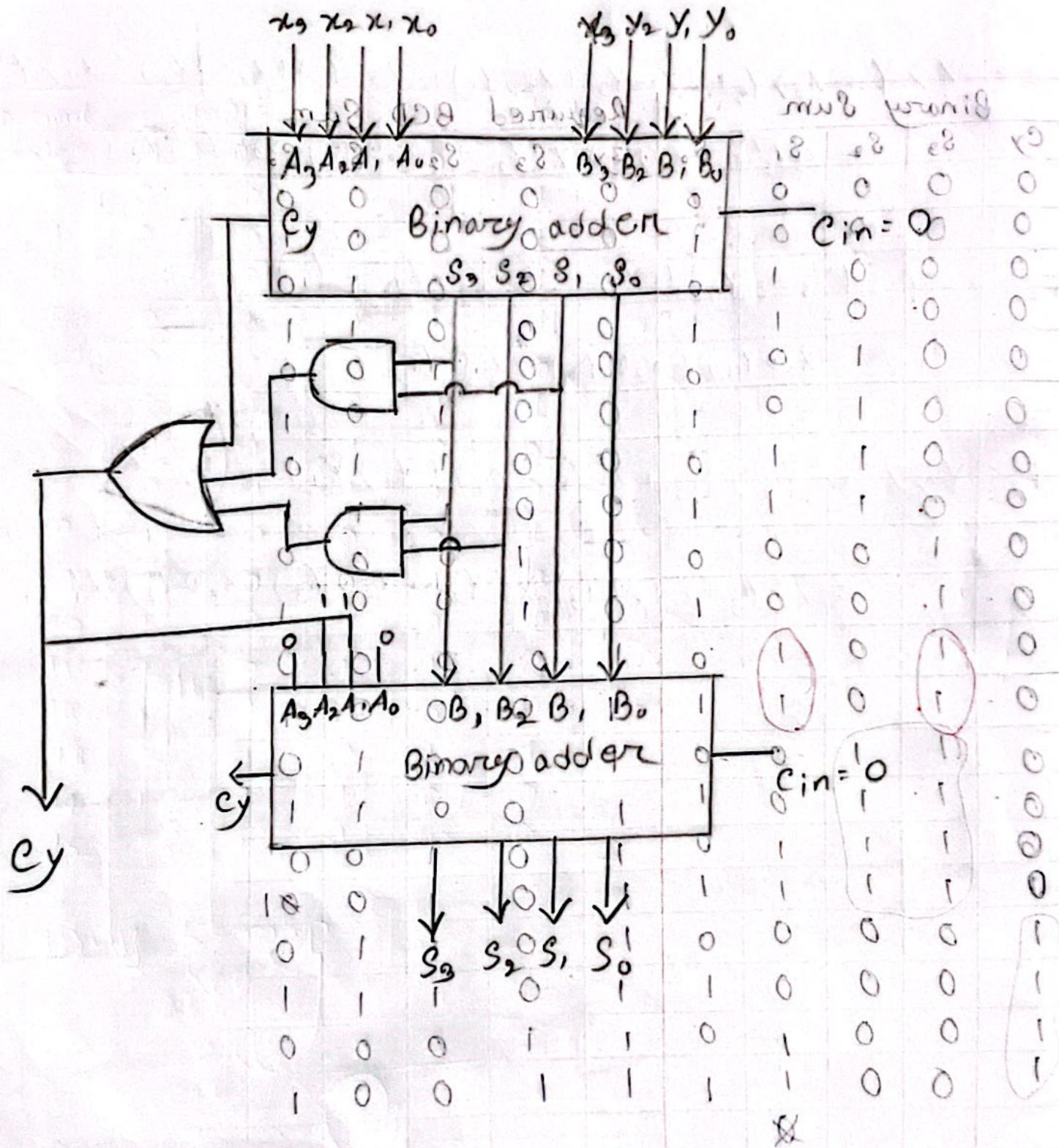

3(b)

state table

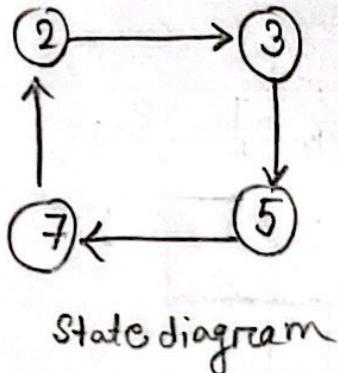

	Present State			Next State			Deciml
	Q_3	Q_2	Q_1	Q_3	Q_2	Q_1	Value
0	1	0	0	0	0	1	1
0	1	1	0	1	0	0	2
1	0	0	1	1	1	1	3
1	1	1	1	0	1	0	4
0	0	0	0	1	0	0	5
1	1	0	0	1	1	0	6
0	0	1	0	0	1	0	7
1	0	1	1	1	1	1	8

we need 3 D flip flop

Excitation Map

Present State			Next State			FF's input		
Q_3	Q_2	Q_1	Q_3	Q_2	Q_1	D_3	D_2	D_1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	1
1	0	1	1	1	1	1	1	1
1	1	1	0	1	0	0	1	0

FF's input equation

Q_3	Q_2	Q_1	D_3
0	0	0	1
1	1	0	1

Q_3	Q_2	Q_1	D_2
0	0	0	1
1	1	0	1


Q_3	Q_2	Q_1	D_1
0	0	1	1
1	1	0	1

$$\begin{aligned}
 D_3 &= Q_3 Q_2' Q_1 + Q_3' Q_2 Q_1 \\
 &= Q_1 (Q_3 Q_2' + Q_3' Q_2) \\
 &= Q_1 (Q_3 \oplus Q_2)
 \end{aligned}$$

$$D_2 = Q_3 Q_1 + Q_3' Q_2 Q_1' \quad D_1 = Q_3 Q_2' Q_1 + Q_3 Q_2$$

$$F = Q_3 D_3 + Q_3' D_2 + Q_3 D_1$$

Digital logic went wrong Diffr

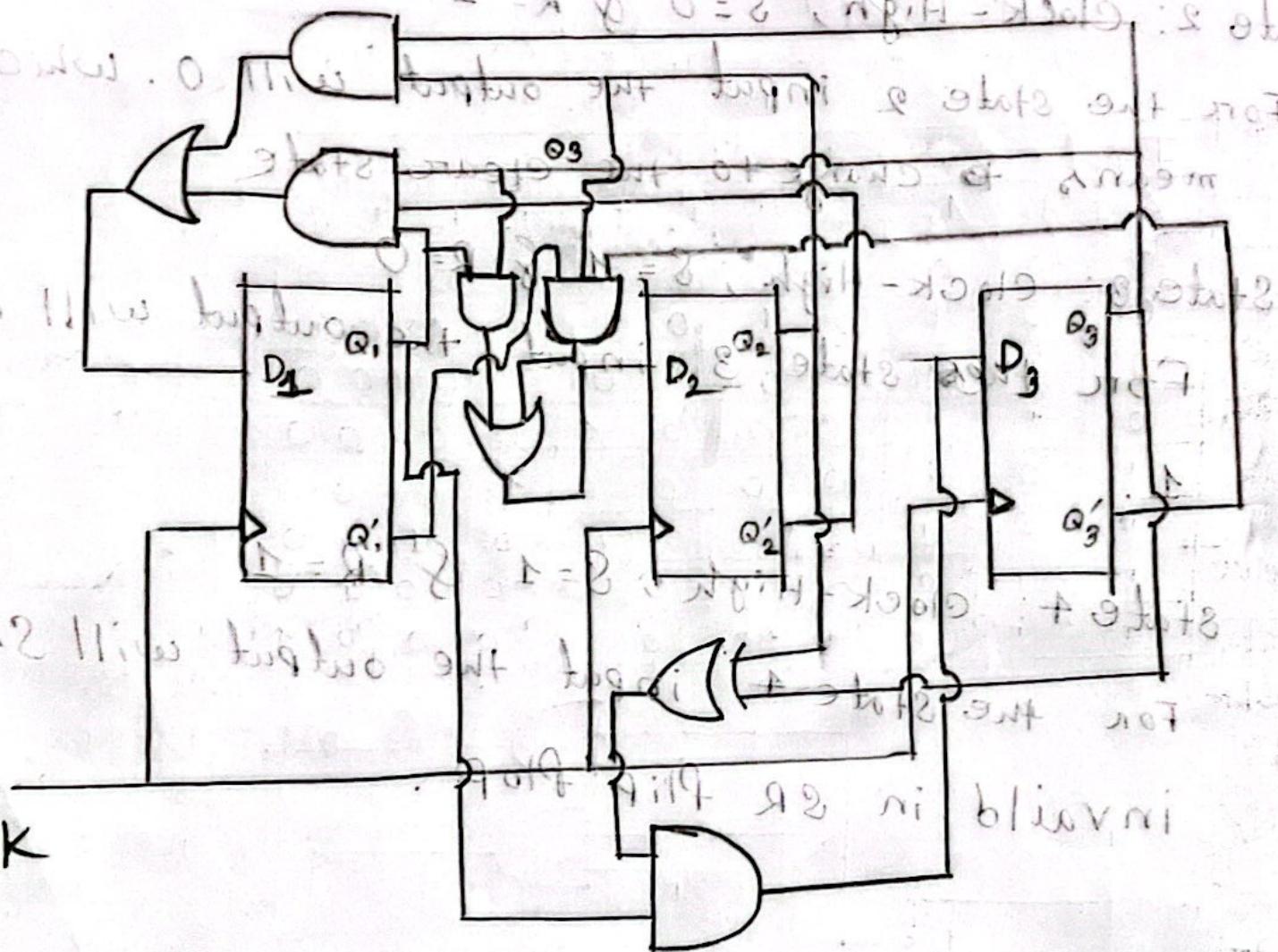

4@

Q3

3 bit + 3 bit

decimal value	input				output	
	A	B	C	D	E	F
0	0	0	0	0	1	0
1	0	0	1	0	1	0
2	0	0	1	1	0	1
3	0	0	1	1	1	1
4	0	1	0	0	0	
5	0	1	0	1	1	
6	0	1	1	0	0	
7	0	1	1	1	0	
8	1	0	0	0	0	1
9	1	0	0	1	0	0
10	1	0	1	0	1	0
11	1	0	1	1	0	1
12	1	1	0	0	0	1
13	1	1	0	1	0	1
14	1	1	1	0	0	0
15	1	1	1	1	0	0

using K-map


		CD	00	01	11	10
AB		00	(1)	1	1	1
	01	01		(1)		
	11	11				
	10	10				

$$F = B'C'D' + A'B' + BC'D$$

Logic diagram draw করতে হবে।

$$(A'B + A'B')D + A'B'E = D$$

D

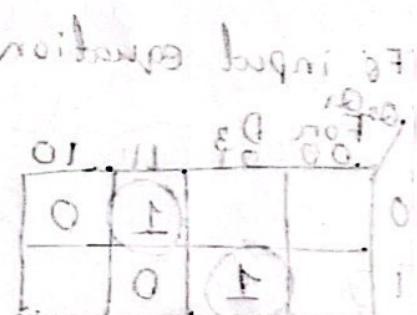


$$(A'B + A'B')D + A'B'E = D$$

$$(A'B + A'B')D + A'B'E =$$

$$(A'B + A'B')D + A'B'E =$$

4.(b)

S_1	S_0	Register operation
0	0	No Change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

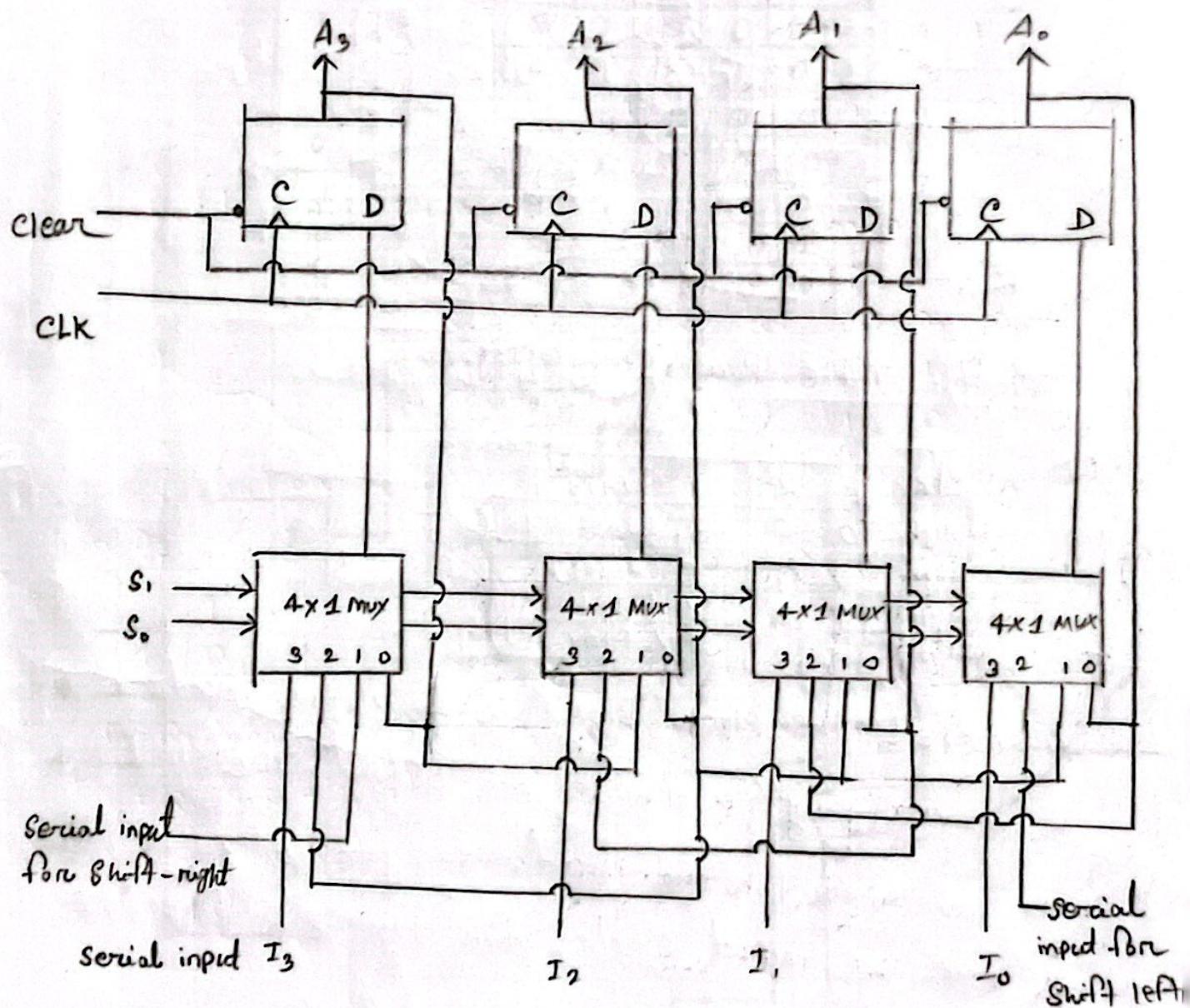


5. @

Q. 3

start back from 909 917 92


Input			I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

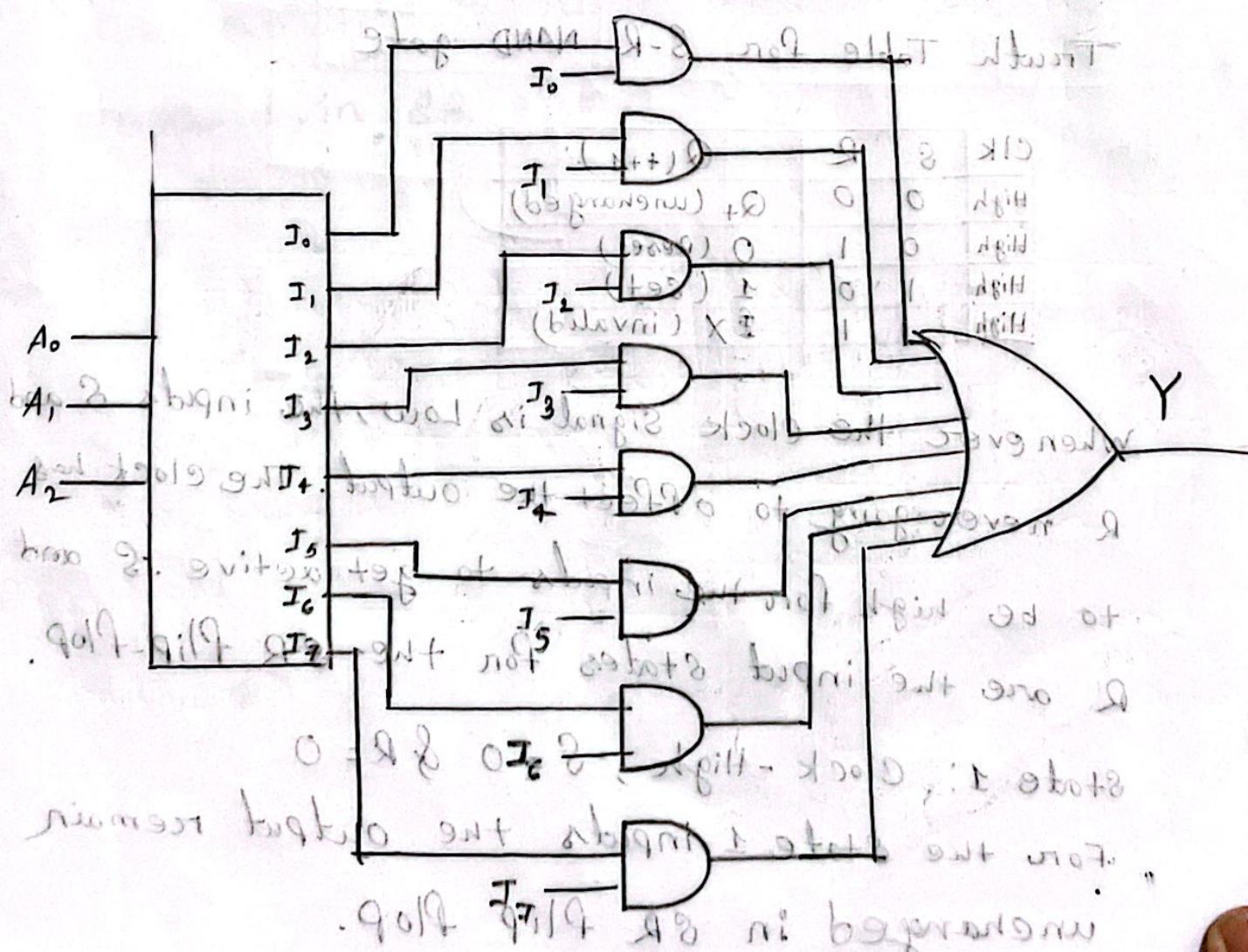

5.(b)

SR flip-flop using Nand gate

bognI

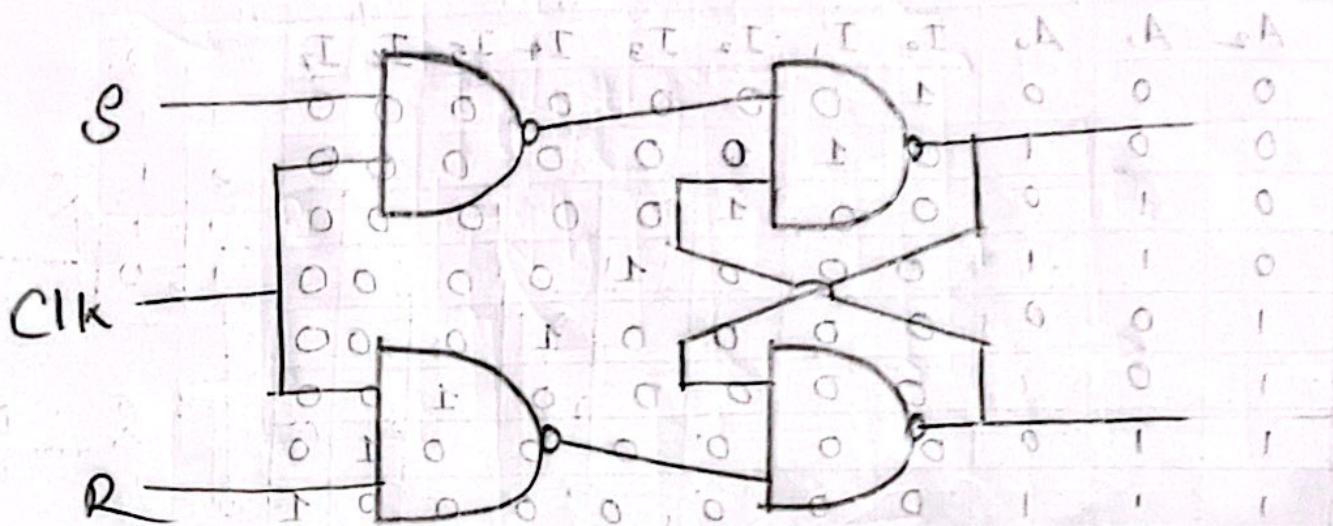

Truth Table for S-R NAND gate

Clk	S	R	$Q_{(++1)}$
High	0	0	Q_+ (unchanged)
High	0	1	0 (Reset)
High	1	0	1 (Set)
High	1	1	X (invalid)

Whenever the clock signal is Low, the inputs S and R never going to affect the output. The clock has to be high for the inputs to get active. S and R are the input states for the SR flip-flop.

State 1: Clock - High, $S = 0$ & $R = 0$

For the state 1 inputs the output remain unchanged in SR flip flop.

State 2: Clock-High, S=0 & R=1

For the state 2 input the output will 0. which means to change to the clear state


State 3: Clock-High, S=1 & R=0

For this state 3 input the output will be 1.

State 4: Clock-High, S=1 & R=1

For the state 4 input the output will shown invalid. in SR flip flop.

6. ②

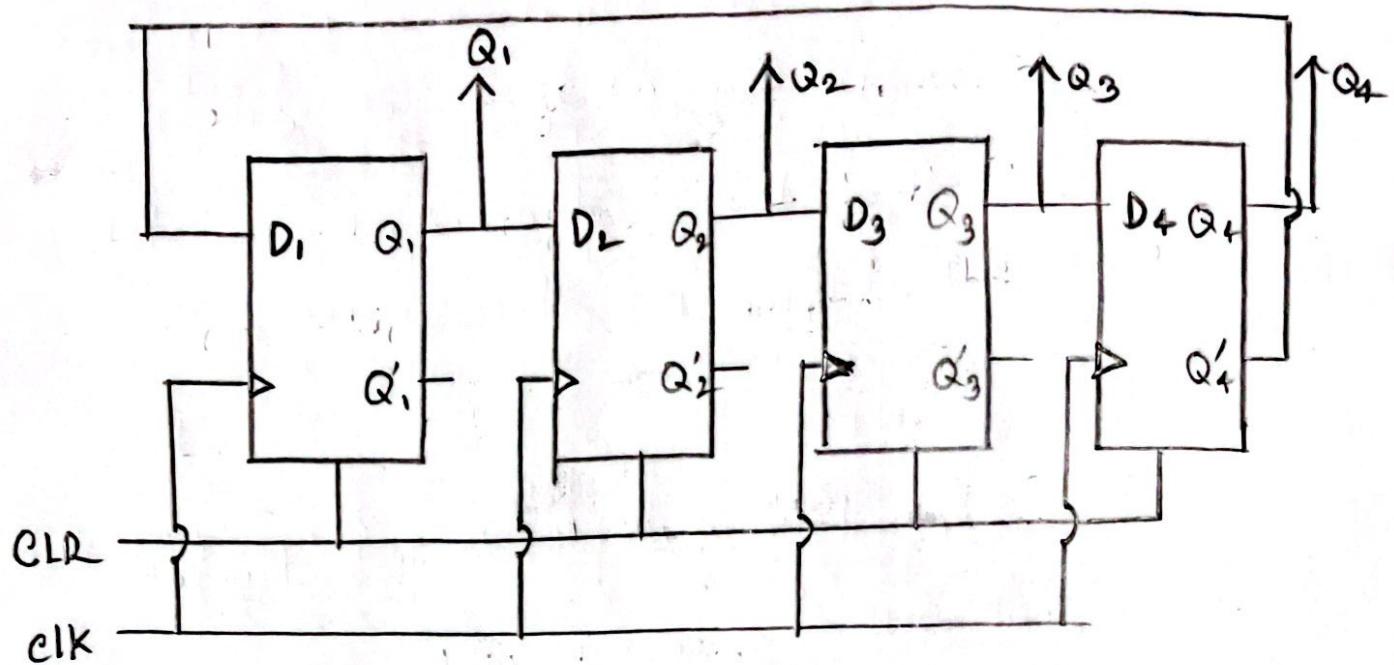

clock pulse No	Q ₁	Q ₂	Q ₃	Q ₄
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	①

6.(b)

$$S_1 = A_1 \oplus B_1$$

$$S_1 = P_1 \oplus C_1$$

$$= P_1 \oplus 0 \quad [\text{initial carry } C_1 = 0]$$

$$= A_1 \oplus B_1$$

$$C_1 = 0$$

$$S_2 = P_2 \oplus C_2$$

$$C_2 = G_2 + P_2 C_1$$

$$= (A_2 \oplus B_2) \oplus A_1 B_1 \quad = A_2 B_2 \quad [\text{initial carry } C_1 = 0]$$

$$C_3 = G_3 + P_3 C_2$$

$$= A_2 B_2 + [(A_2 \oplus B_2) A_1 B_1]$$

$$S_3 = P_3 \oplus C_3$$

$$= (A_3 \oplus B_3) \oplus [A_2 B_2 + (A_2 \oplus B_2) A_1 B_1]$$

$$C_4 = G_4 + P_4 C_3$$

$$= A_3 B_3 + (A_3 \oplus B_3) [A_2 B_2 + (A_2 \oplus B_2) A_1 B_1]$$

$$S_4 = P_4 \oplus C_4$$

$$= (A_4 \oplus B_4) + [A_3 B_3 + (A_3 \oplus B_3) [A_2 B_2 + (A_2 \oplus B_2) A_1 B_1]]$$

$$C_5 = G_5 + P_5 C_4$$

$$= A_4 B_4 + (A_4 \oplus B_4) [A_3 B_3 + (A_3 \oplus B_3) [A_2 B_2 + (A_2 \oplus B_2) A_1 B_1]]$$

7.(b)

$$F_1 \circ: X > Y = X_3 > Y_3 + (X_3 = Y_3)(X_2 > Y_2) + (X_3 = Y_3)(X_2 = Y_2)(X_1 > Y_1)$$
$$= X_3 Y_3' + (X_3 \odot Y_3) X_2 Y_2' + (X_3 \odot Y_3)(X_2 \odot Y_2) X_1 Y_1'$$

$$F_2: X = Y = (X_3 = Y_3)(X_2 = Y_2)(X_1 = Y_1)$$
$$= (X_3 \odot Y_3)(X_2 \odot Y_2)(X_1 \odot Y_1)$$

$$F_3: Y > X = Y_3 > X_3 + (Y_3 = X_3)(Y_2 > X_2) + (Y_3 = X_3)(Y_2 = X_2)(Y_1 > X_1)$$
$$= X_3' Y_3 + (X_3 \odot Y_3) X_2' Y_2 + (X_3 \odot Y_3)(X_2 \odot Y_2) X_1' Y_1$$

d. F

