



MULTIPLEXER / MUX / DATA SELECTOR

MULTIPLEXERS

- A multiplexer is a combinational circuit that selects one of many input lines (2^n) and directs it to its single output line.
- There are n selection lines whose bit combinations determine which input is selected.
- A multiplexer is also called a data selector, since it selects one of many inputs and steers the binary information to the output line.
- The size of a multiplexer is specified by the number 2^n of its input lines and the single output line. It is then implied that it also contains n selection lines.
- Example: 2X1 MUX, 4X1 MUX, 8X1 MUX, 16X1 MUX etc.



MULTIPLEXERS

4-to-1 MUX

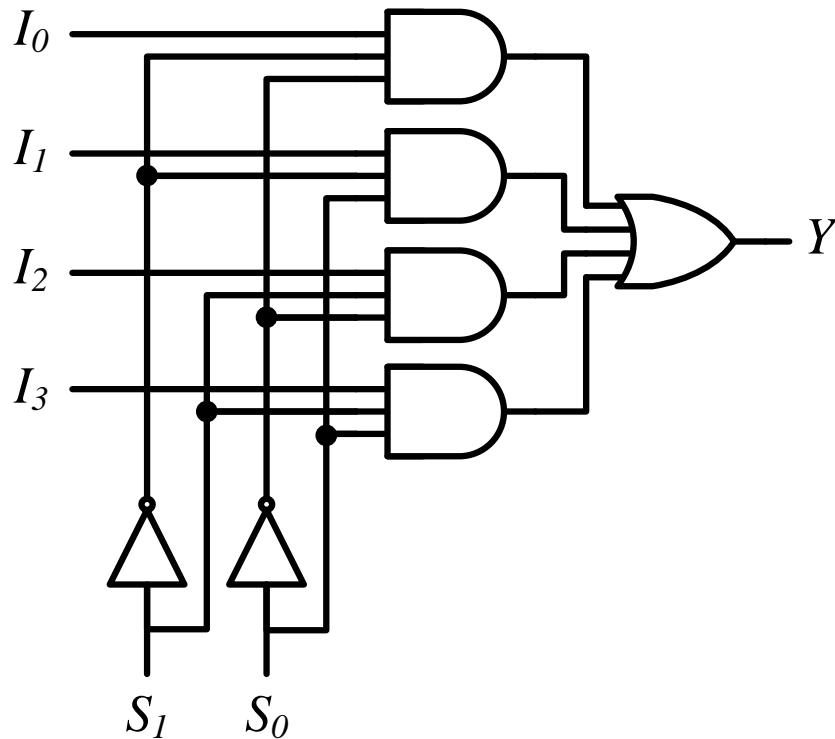


Fig: Logic diagram of a 4X1 MUX

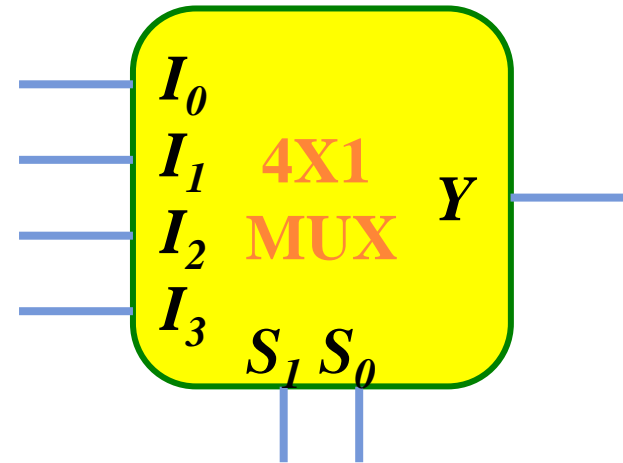


Fig: Block diagram of a 4X1 MUX

Function Table of a 4X1 MUX:

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Output Equation:

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$


USES OF MUX

- It is used for connecting two or more sources to a single destination among computer units.
- It is useful for constructing a common bus system etc.



FUNCTION IMPLEMENTATION USING MUX

- $(n+1)$ variable function can be implemented with $2^n \times 1$ MUX
- Simplify the function in sum of minterms form
- Among $(n+1)$ variables, n variables are used as selector and one variable is connected with input lines

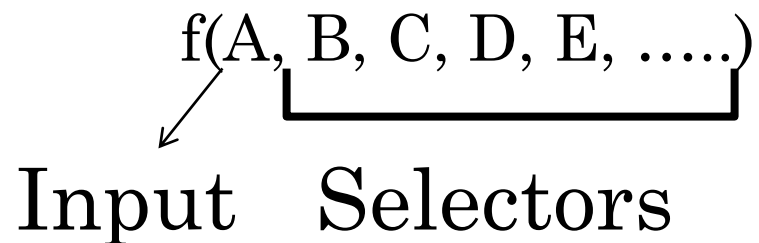

Procedure 1



IMPLEMENTATION USING MULTIPLEXERS:

PROCEDURE 1

$$F(A, B, C) = \sum(1, 3, 5, 6)$$

Steps:

1. Choose the selector variables.
Let's choose,
 - B, C as selector S_1 and S_0
 - A as input line
2. In the first row, list the name of the input lines of the multiplexers horizontally
3. In the second row, list the minterms where A is complemented
4. In the third row, list the minterms where A is uncomplemented




IMPLEMENTATION USING MULTIPLEXERS:

PROCEDURE 1

$$F(A, B, C) = \sum(1, 3, 5, 6)$$

Steps:


5. Circle the minterms for which the function outputs 1
 6. Fourth row presents the multiplexer inputs
 - If the two minterms in a column are not circled, apply 0 to the corresponding multiplexer input
 - If the two minterms in a column are circled, apply 1 to the corresponding multiplexer input
 - If the bottom minterm is circled and the top is not circled, apply A to the corresponding multiplexer input
 - If the top minterm is circled and the bottom is not circled, apply A' to the corresponding multiplexer input
- 

IMPLEMENTATION USING MULTIPLEXERS: PROCEDURE 1

○ $F(A, B, C) = \sum(1, 3, 5, 6)$

Implementation Table:

MUX input line	I ₀	I ₁	I ₂	I ₃
A'	0	①	2	③
A	4	⑤	⑥	7
Input values	0	1	A	A'

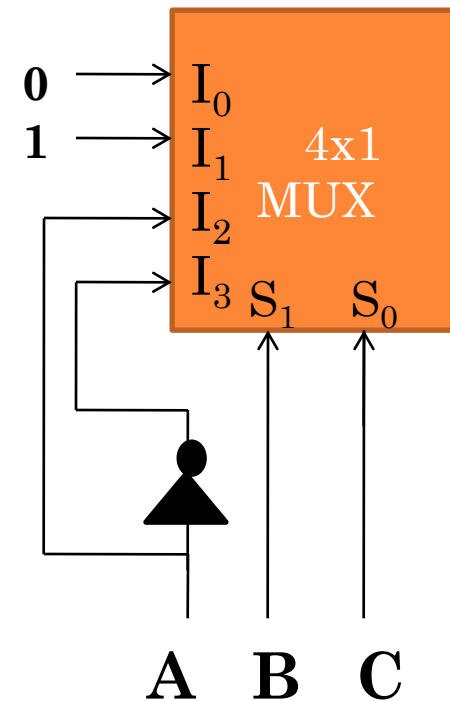

IMPLEMENTATION USING MULTIPLEXERS:


PROCEDURE 1

- $F(A, B, C) = \sum(1, 3, 5, 6)$

What if A, B are the selectors and C goes to input line?

Implementation Table:

MUX input line	I ₀	I ₁	I ₂	I ₃
C'	0	2	4	⑥
C	①	③	⑤	7
Input values	C	C	C	C'

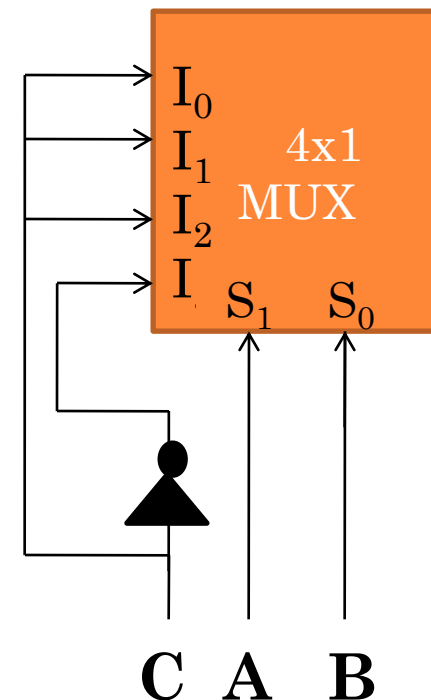

Procedure 2



IMPLEMENTATION USING MULTIPLEXERS:

PROCEDURE 2


- Steps:

1. Complete the truth table from the SOP.
2. The first $n - 1$ variables in the table are applied to the selection inputs of the multiplexer.
3. For each combination of the selection variables, we evaluate the output as a function of the last variable.
4. Apply these values to the data input in proper order.



IMPLEMENTATION USING MULTIPLEXERS: PROCEDURE 2


- Example $F(x, y) = \sum(0, 1, 3)$

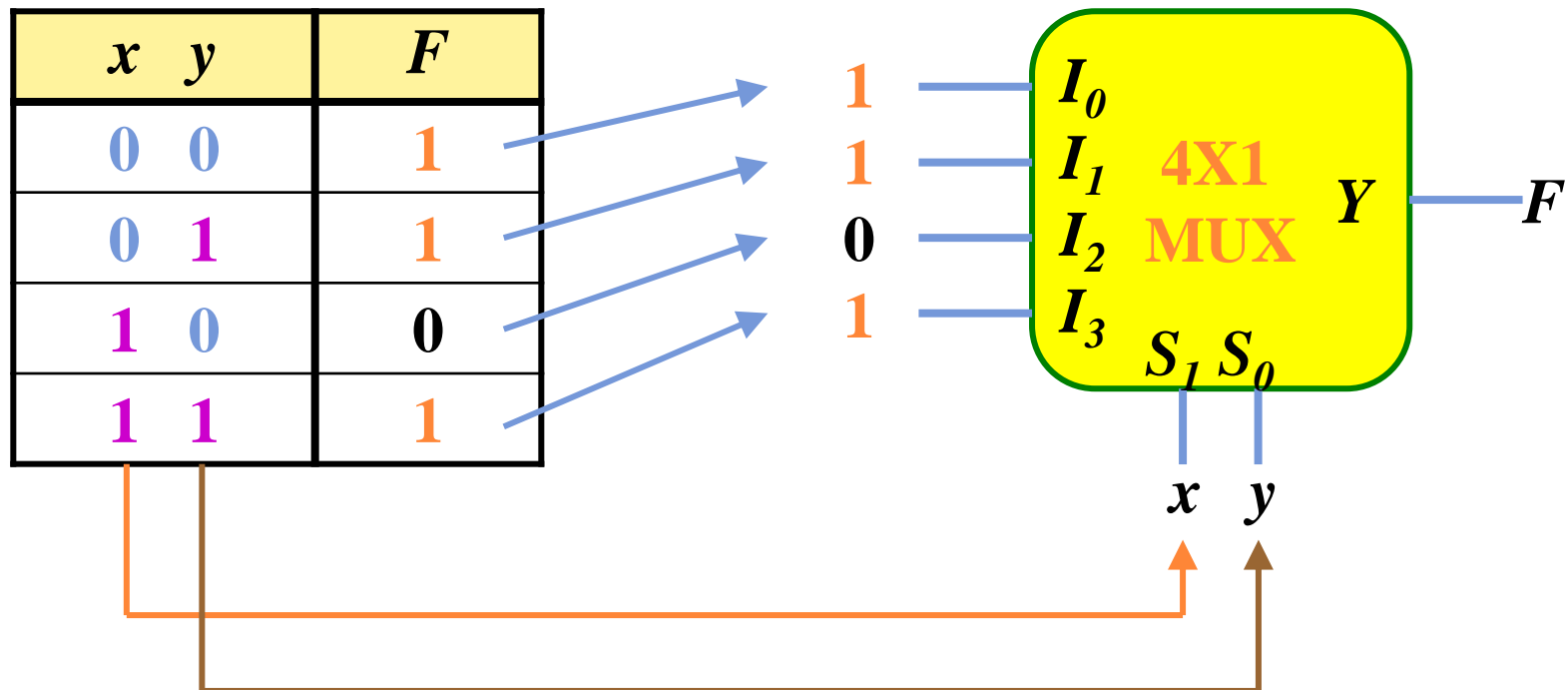

IMPLEMENTATION USING MULTIPLEXERS: PROCEDURE 2

- Example $F(x, y, z) = \sum(1, 2, 6, 7)$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

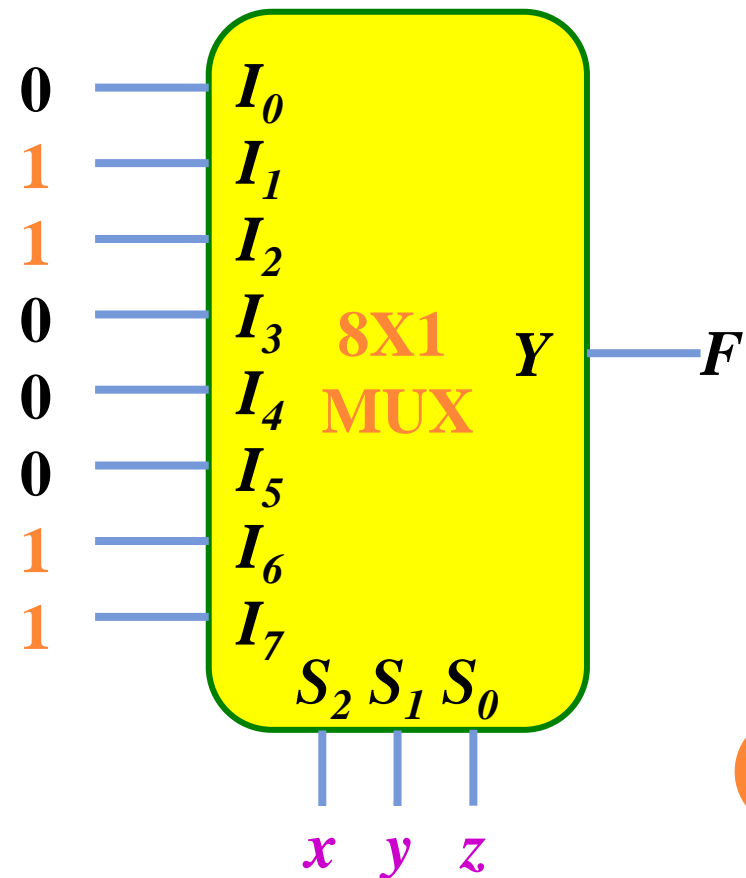

IMPLEMENTATION USING MULTIPLEXERS: PROCEDURE 2

○ $F(x, y, z) = \sum(1, 2, 6, 7)$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$F = z$

$F = \bar{z}$

$F = 0$


$F = z + z' = 1$

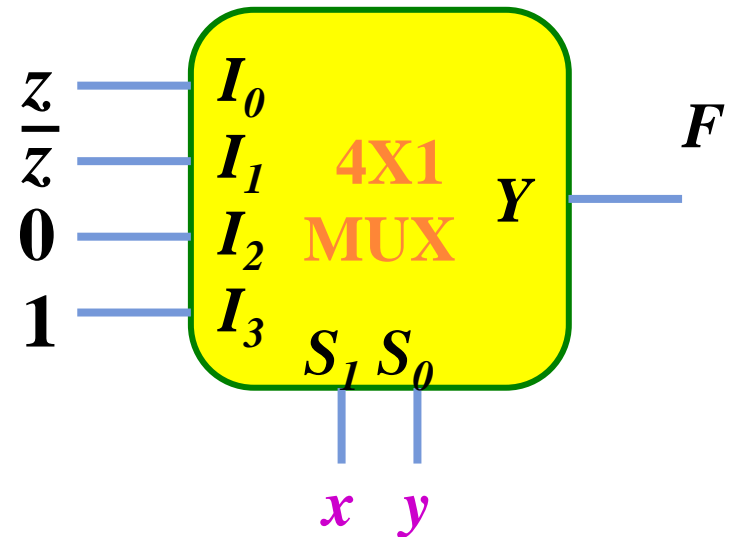

IMPLEMENTATION USING MULTIPLEXERS: PROCEDURE 2

○ $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$

A	B	C	D	F	
0	0	0	0	0	} $F = D$
0	0	0	1	1	
0	0	1	0	0	} $F = D$
0	0	1	1	1	
0	1	0	0	1	} $F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	} $F = 0$
0	1	1	1	0	
1	0	0	0	0	} $F = 0$
1	0	0	1	0	
1	0	1	0	0	} $F = D$
1	0	1	1	1	
1	1	0	0	1	} $F = 1$
1	1	0	1	1	
1	1	1	0	1	} $F = 1$
1	1	1	1	1	

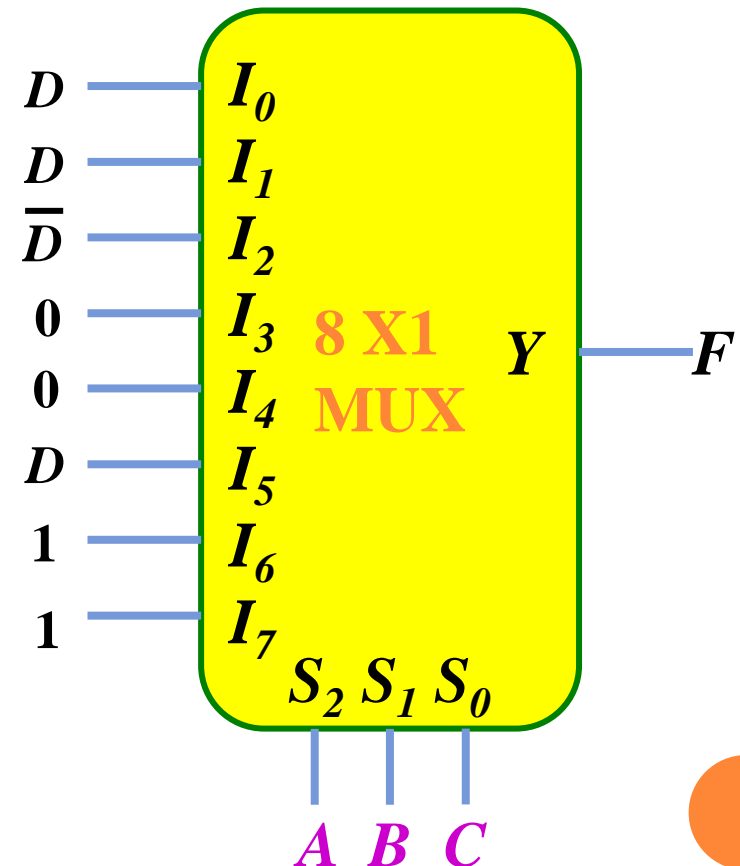


PROCEDURE 1 VS PROCEDURE 2

- Among the function variables, if the first or some middle variable other than the last one is to be used in input line then procedure 1 is preferable.



MULTIPLEXER EXPANSION

4-TO-1 MUX USING 2-TO-1 MUX

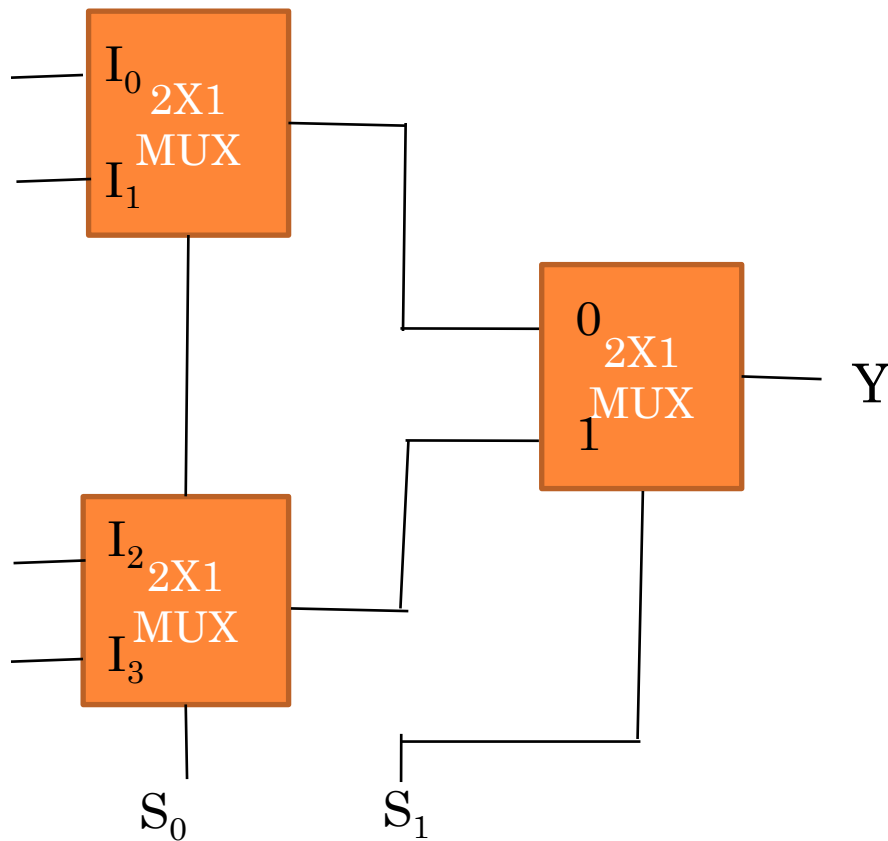


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3



MULTIPLEXER EXPANSION

4-TO-1 MUX USING 2-TO-1 MUX

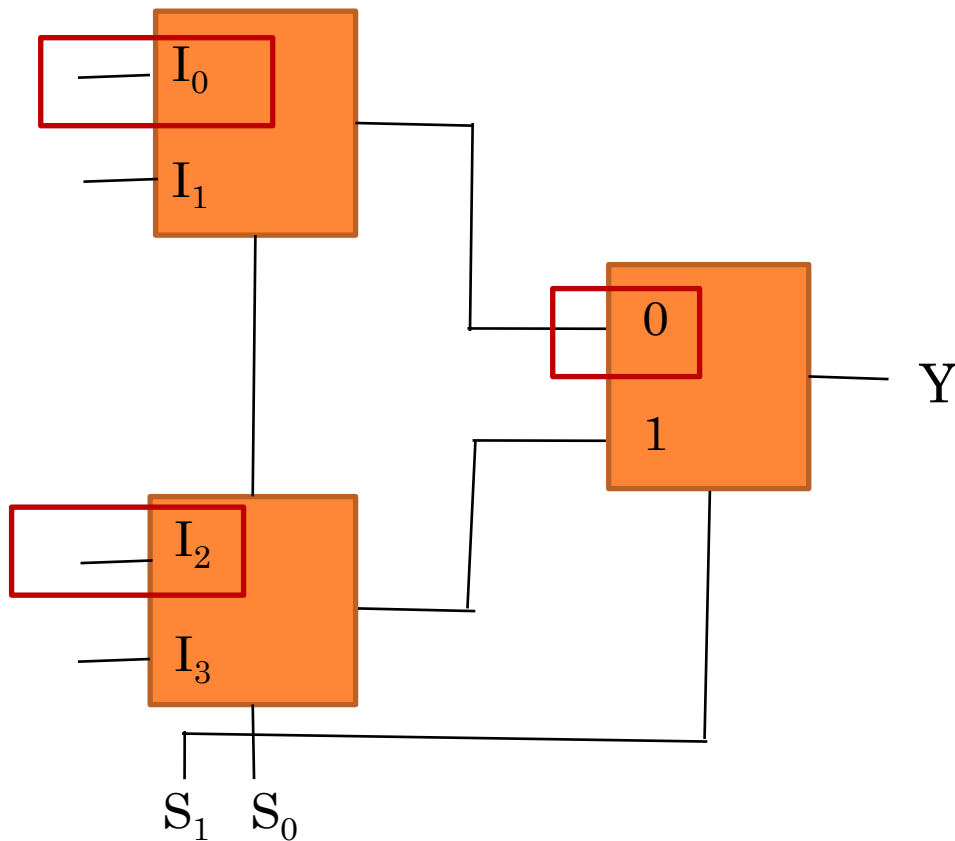


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3



MULTIPLEXER EXPANSION

4-TO-1 MUX USING 2-TO-1 MUX

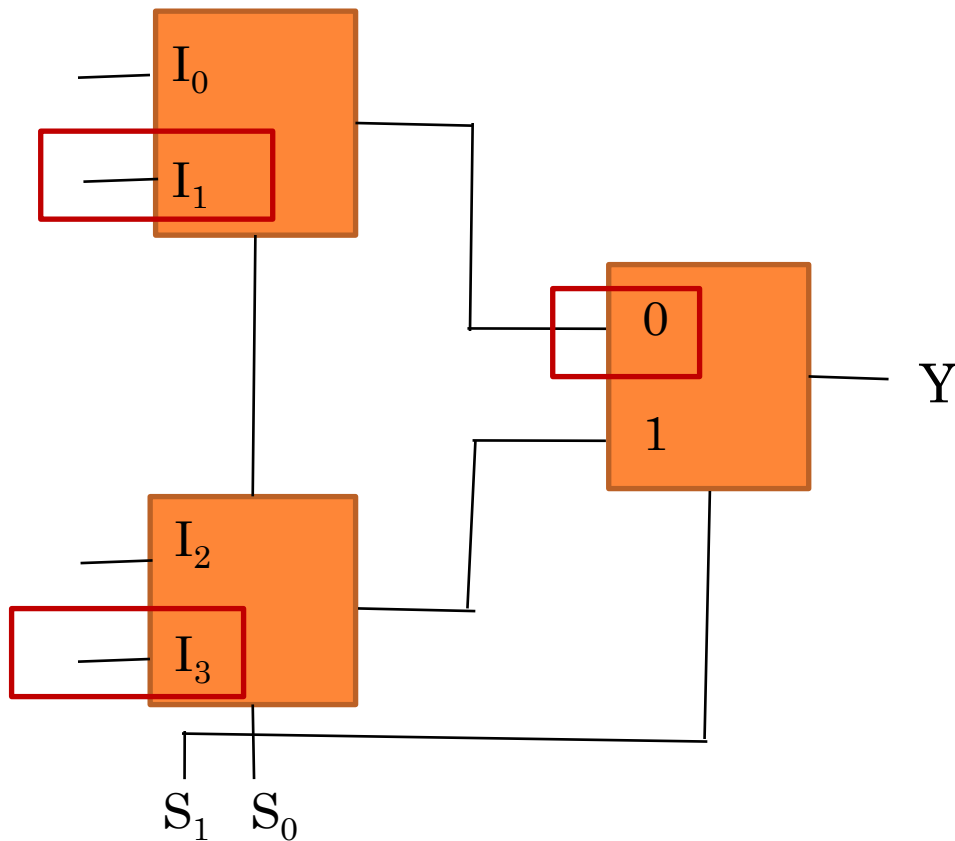


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3



MULTIPLEXER EXPANSION

4-TO-1 MUX USING 2-TO-1 MUX

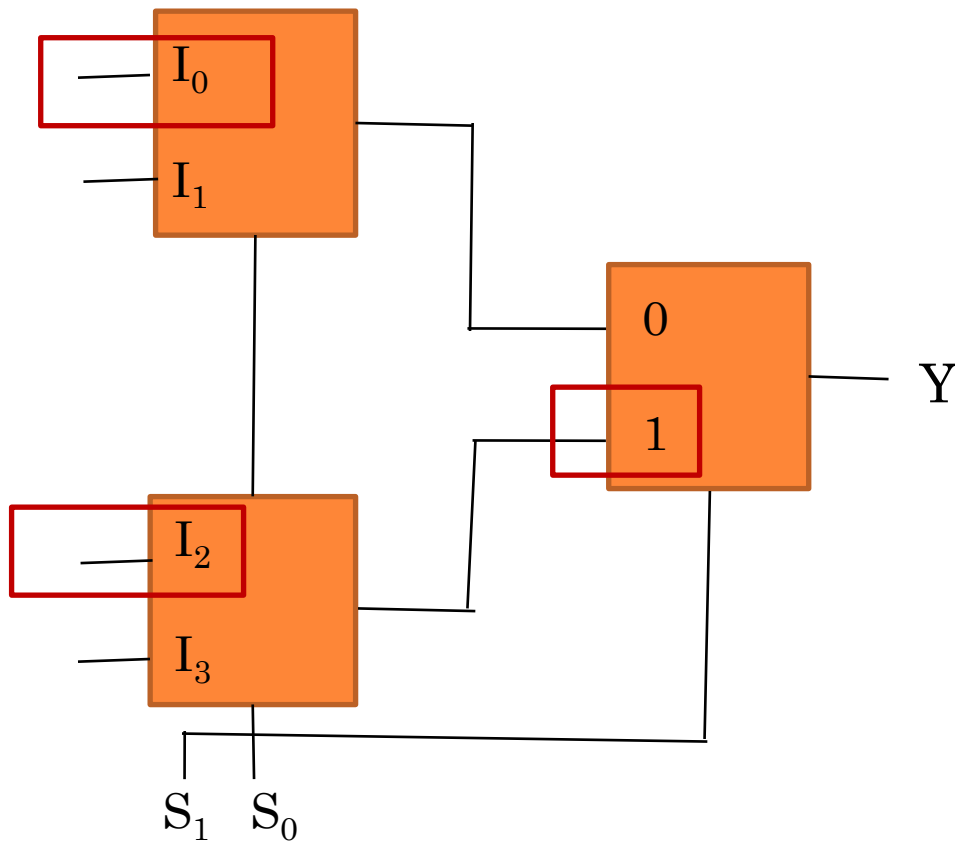


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3



MULTIPLEXER EXPANSION

4-TO-1 MUX USING 2-TO-1 MUX

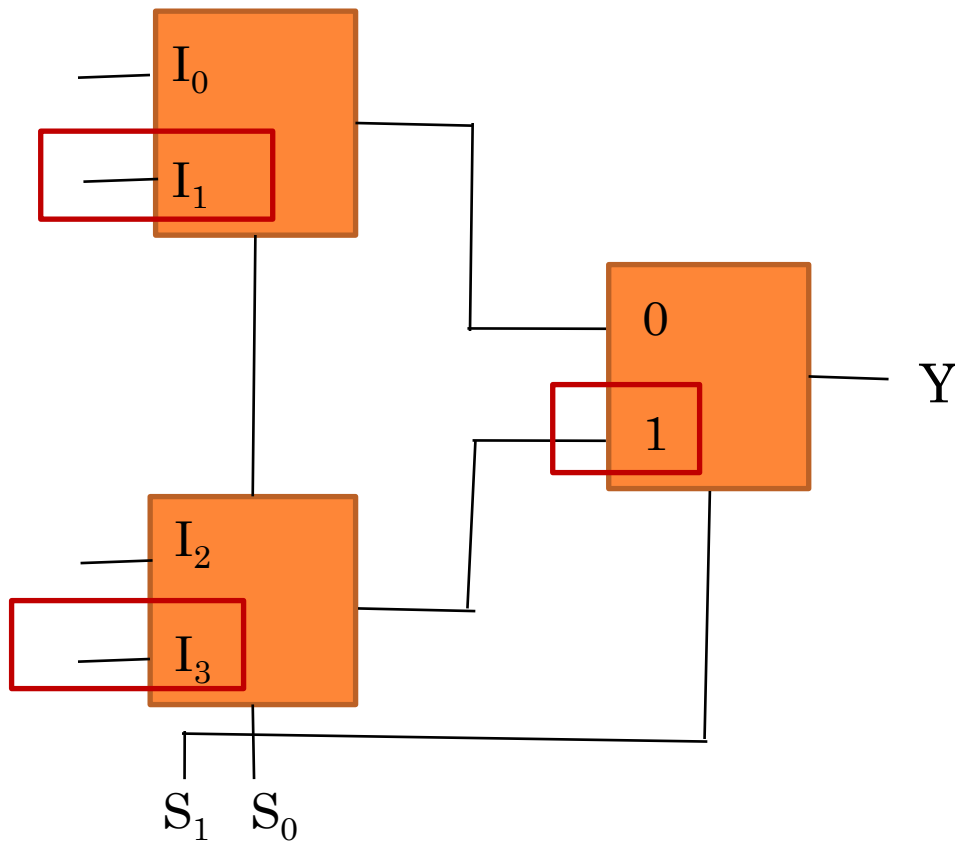


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3




MULTIPLEXER EXPANSION [SELF STUDY]

8-TO-1 MUX USING DUAL 4-TO-1 MUX

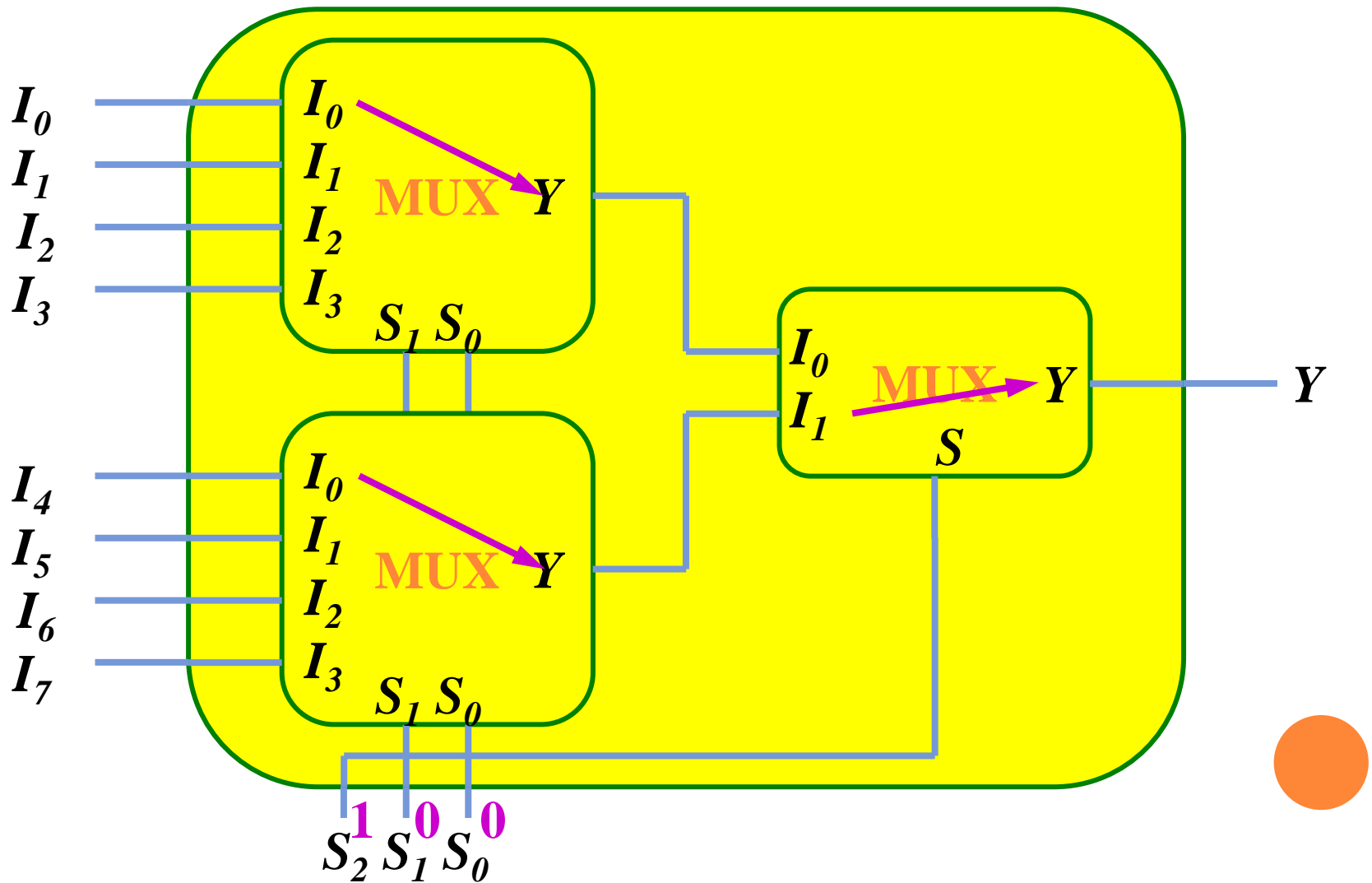



MULTIPLEXERS

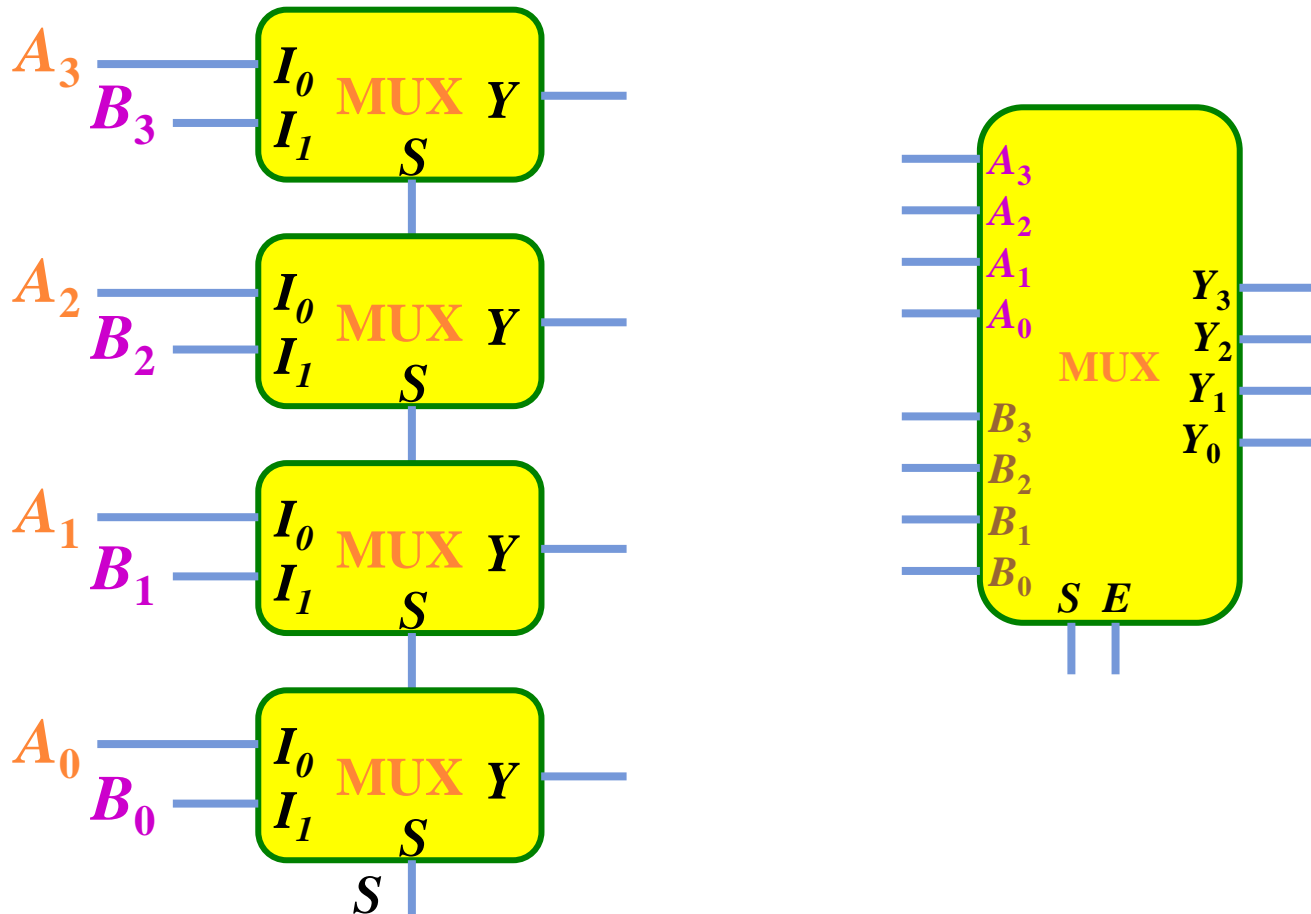- Quad 2-to-1 MUX:
Four 2x1 MUX can be used simultaneously



MULTIPLEXERS



Quad 2-to-1 MUX

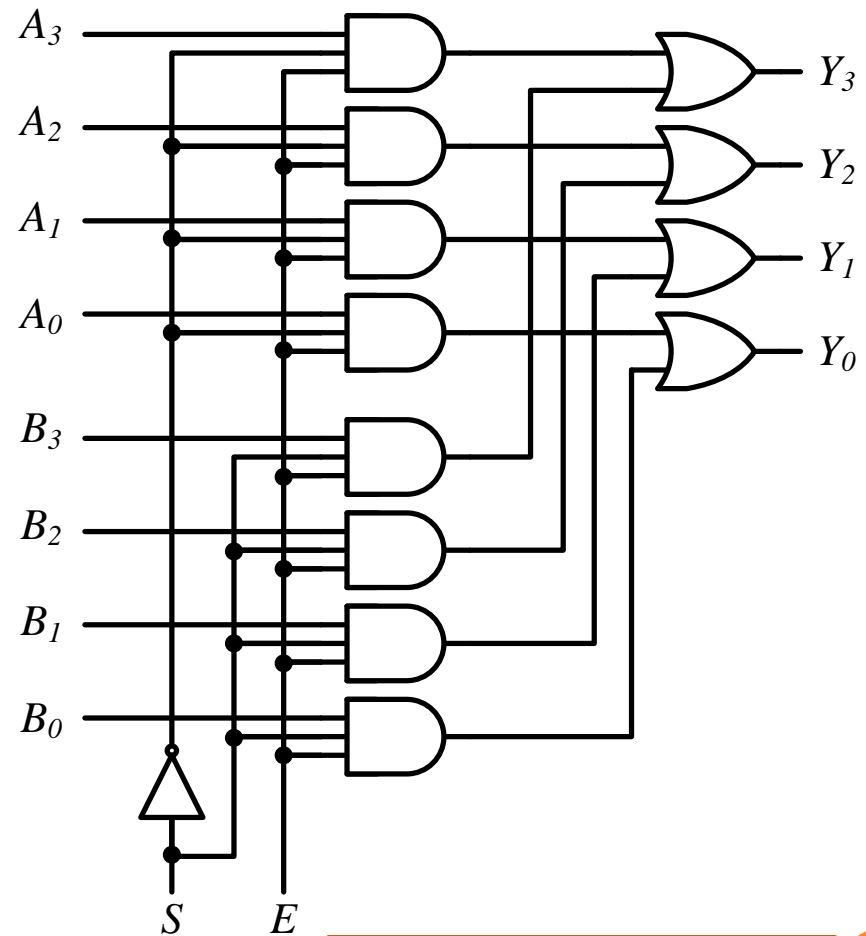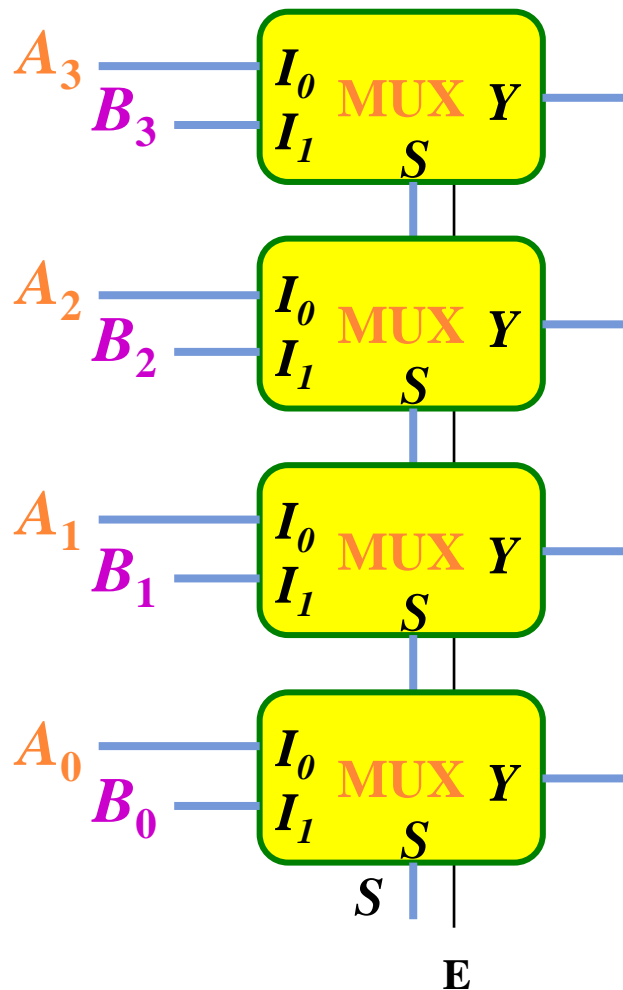

Active **High** Enable:
The output is
enabled when $E=1$

MULTIPLEXERS

Quad 2-to-1 MUX

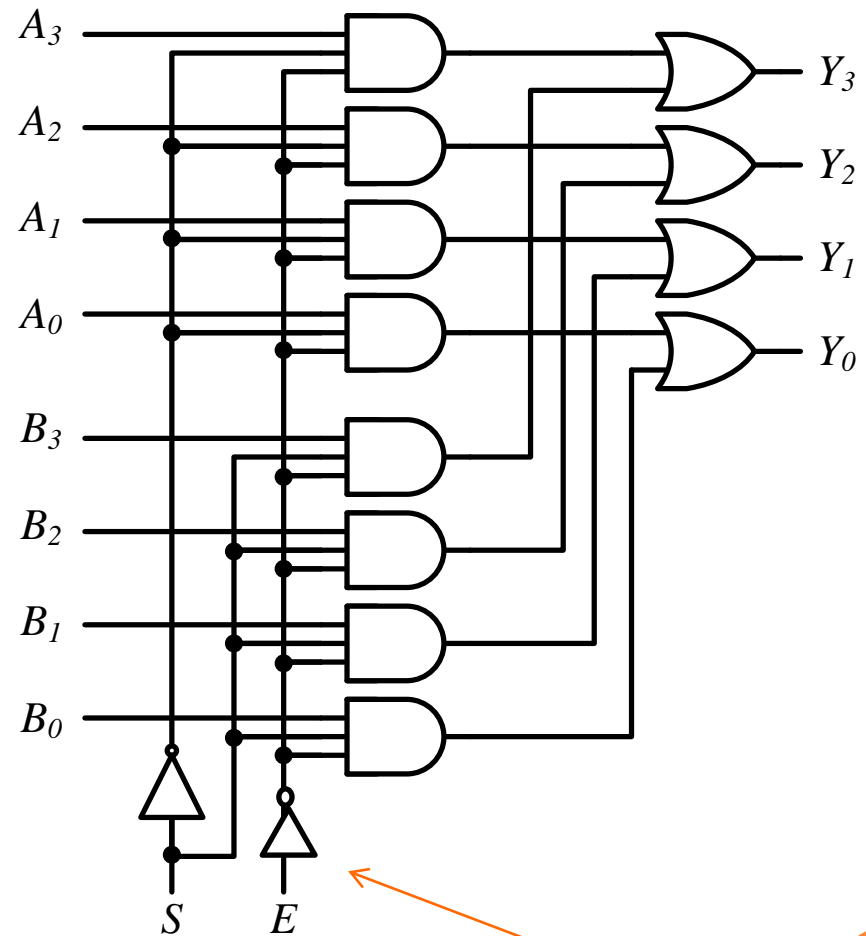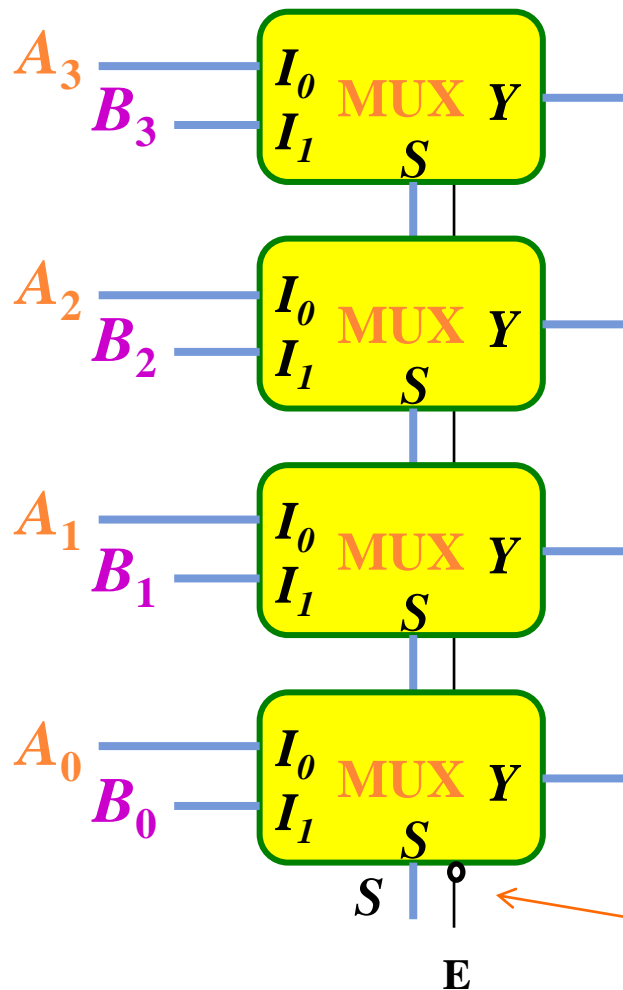

Active **Low** Enable:
The output is
enabled when $E=0$